


Exercise 7.3

(a) **xor**

The datapath does not require any changes to its interfaces. Only the ALU needs to be modified: we add another input to the multiplexer and N 2-bit XOR gates within the ALU. We also update the ALU Decoder truth table / logic. The Main Decoder truth table need not be updated because it already supports R-type instructions. These changes are shown below.

Modified ALU operations to support xor

$ALUControl_{2:0}$	Function
000	add
001	subtract
010	and
011	or
100	xor
101	SLT

 


Modified ALU Decoder truth table to support xor

<i>ALUOp</i>	<i>funct3</i>	<i>op5, funct7₅</i>	<i>ALUControl</i>	Instruction
00	x	x	000 (add)	lw, sw
01	x	x	001 (subtract)	beq
10	000	00, 01, 10	000 (add)	add, addi
	000	11	001 (subtract)	sub
	010	x	101 (set less than)	slt, slti
	100	x	100 (xor)	xor, xori
	110	x	011 (or)	or, ori
	111	x	010 (and)	and, andi

(b) sll

The overall datapath (interfaces and units) need not be changed. We only modify the ALU and the ALU Decoder, as shown below. We add a shifter and expand the multiplexer inside the ALU.

Modified ALU to support sll

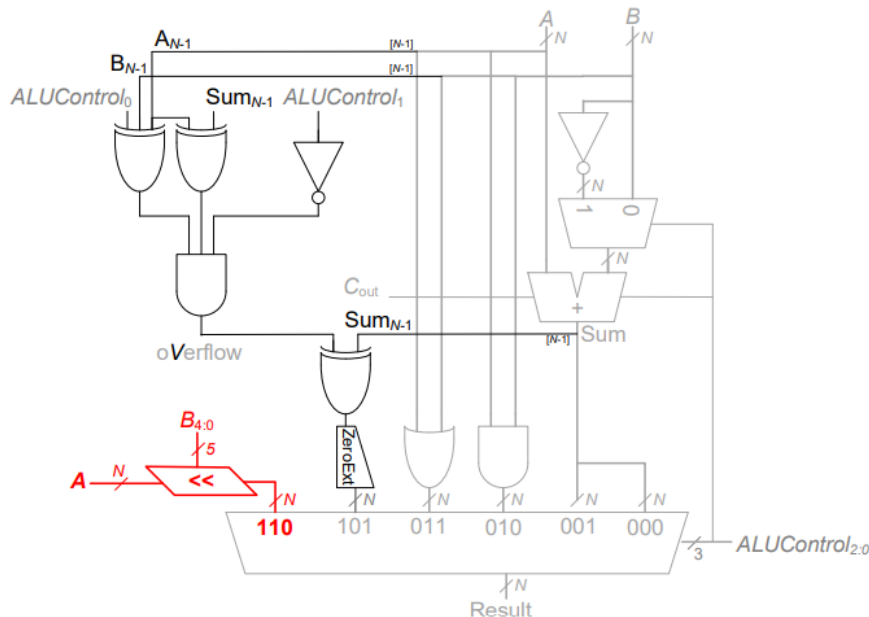

Modified ALU operations to support sll

<i>ALUControl_{2:0}</i>	Function
000	add
001	subtract
010	and
011	or
101	SLT
110	sll


Modified ALU Decoder truth table to support srl

<i>ALUOp</i>	<i>funct3</i>	<i>op₅, funct7₅</i>	<i>ALUControl</i>	<i>Instruction</i>
00	x	x	000 (add)	lw, sw
01	x	x	001 (subtract)	beq
10	000	00, 01, 10	000 (add)	add, addi
	000	11	001 (subtract)	sub
	001	x	110 (shift left logical)	sll, slli
	010	x	101 (set less than)	slt, slti
	110	x	011 (or)	or, ori
	111	x	010 (and)	and, andi

(c) srl

The overall datapath (interfaces and units) need not be changed. We only modify the ALU and the ALU Decoder, as shown below. We add a shifter and expand the multiplexer inside the ALU.

Modified ALU to support srl

 

Modified ALU operations to support srl

<i>ALUControl_{2:0}</i>	<i>Function</i>
000	add
001	subtract
010	and
011	or
101	SLT
111	srl

Modified ALU Decoder truth table to support srl

ALUOp	func3	op5, func7 ₅	ALUControl	Instruction
00	x	xx	000 (add)	lw, sw
01	x	xx	001 (subtract)	beq
10	000	00, 01, 10	000 (add)	add, addi
	000	11	001 (subtract)	sub
	001	x0	111 (shift right logical)	srl, srli
	010	xx	101 (set less than)	slt, slti
	110	xx	011 (or)	or, ori
	111	xx	010 (and)	and, andi


(d) bne

bne is the opposite of beq. beq and bne can be identified by **func3₀**, which is high when bne is the instruction. To implement, we simply need to change the control unit to branch when *Zero* is 0 and bne is the instruction or when *Zero* is 1 and beq is the instruction. This is easily achieved with *Zero* XOR **func3₀**.

Main Decoder truth table enhanced to support bne

Instruction	Opcode	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
Lw	0000011	1	00	1	0	01	0	00	0
Sw	0100011	0	01	1	1	xx	0	00	0
R-type	0110011	1	xx	0	0	00	0	10	0
beq/ bne	1100011	0	10	0	0	xx	1	01	0
Addi	0010011	1	00	0	0	00	0	10	0
Jal	1101111	1	11	x	0	10	0	xx	1

Enhanced control unit for bne

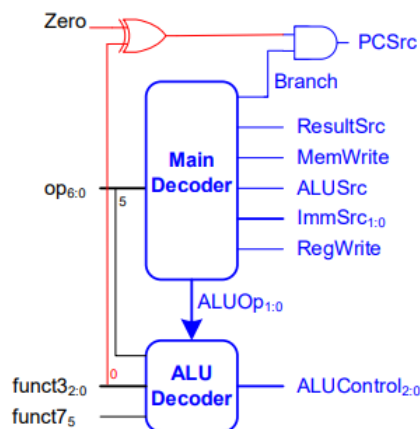

(a) `lui`
First, we update the immediate Extend unit to support `lui`.

First, we update the immediate Extend unit to support `lui`.

<i>ImmSrc</i>	<i>ImmExt</i>	Type	Description
000	{{20{ <i>Instr</i> [31]}}, <i>Instr</i> [31:20]}	I	12-bit signed immediate
001	{{20{ <i>Instr</i> [31]}}, <i>Instr</i> [31:25], <i>Instr</i> [1:7]}	S	12-bit signed immediate
010	{{20{ <i>Instr</i> [31]}}, <i>Instr</i> [7], <i>Instr</i> [30:25], <i>Instr</i> [11:8], 1'b0}	B	13-bit signed immediate
011	{{12{ <i>Instr</i> [31]}}, <i>Instr</i> [19:12], <i>Instr</i> [20], <i>Instr</i> [30:21], 1'b0}	J	21-bit signed immediate
100	<i>Instr</i>[31:12], 12'b0}	U	20-bit signed immediate

Next, we modify the datapath by increasing the width of the *ImmSrc* control signal to 3 bits and by making 0 an option for the ALU's top input (*SrcA*).


Instruction	Opcode	RegWrite	ImmSrc	ALUSrcA	ALUSrcB	MemWrite	ResultSrc	Branch	ALUOp	Jump
lw	0000011	1	000	0	1	0	01	0	00	0
sw	0100011	0	001	0	1	1	xx	0	00	0
R-type	0110011	1	xxx	0	0	0	00	0	10	0
beq	1100011	0	010	0	0	0	xx	1	01	0
I-type ALU	0010011	1	000	0	0	0	00	0	10	0
jal	1101111	1	011	x	x	0	10	0	xx	1
lui	0110111	1	100	1	1	0	00	0	xx	0

(c) `lbu`

To implement `lbu` we create a load/store unit (LSU) within the controller that outputs a new signal *LoadType*. The LU takes in **funct3** and outputs *LoadType*. When *LoadType* is 0, it is an `lbu` instruction, and a zero-extended byte of the *ReadData* bus (selected using the two least significant bits of the address) is sent to the ResultSrc multiplexer.

Otherwise, *ReadData* is sent. We add the following to the datapath: the new signal, *LoadType*, zero-extension unit, 4:1 multiplexer to select the byte within the *ReadData* word, and a *LoadType* multiplexer.


Enhanced datapath to support `lbu`

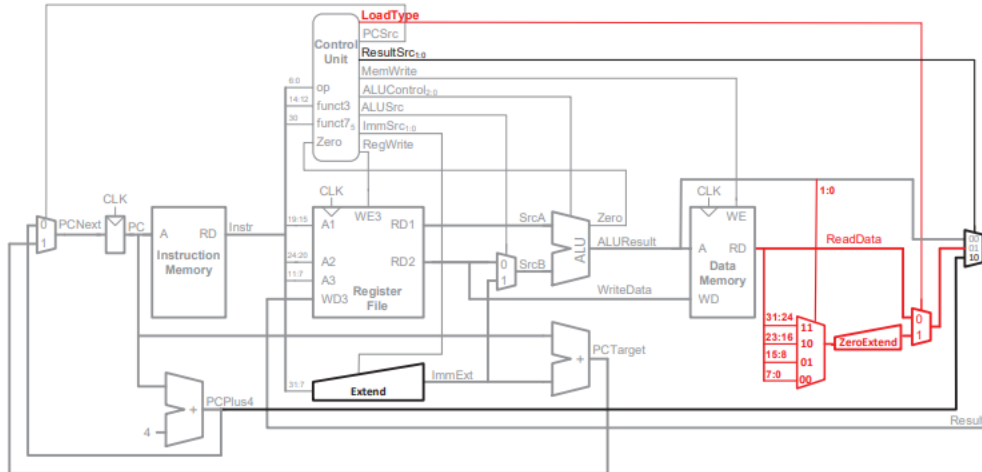

Main Decoder truth table enhanced to support `lbu`

Instruction	Opcode	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
<code>lw</code> / <code>lbu</code>	0000011	1	000	1	0	01	0	00	0
<code>sw</code>	0100011	0	001	1	1	xx	0	00	0
R-type	0110011	1	xxx	0	0	00	0	10	0
<code>beq</code>	1100011	0	010	0	0	xx	1	01	0
I-type ALU	0010011	1	000	0	0	00	0	10	0
<code>jal</code>	1101111	1	011	x	0	10	0	xx	1

Enhanced control unit for `lbu`

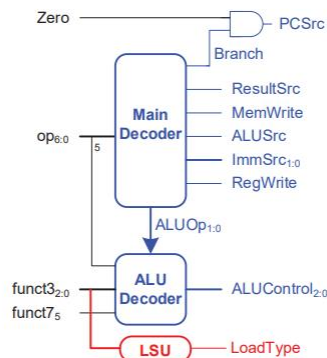


LSU truth table to support `lbu`

funct3	LoadType	Instruction
010	0	<code>lw</code>
100	1	<code>lbu</code>


(h) jalr

The jalr instruction jumps to the target address calculated by adding **rs1** and the sign-extended 12-bit immediate. It also writes PC+4 to **rd**. The datapath already supports these calculations: the ALU can perform **rs1 + ImmExt**; and PC+4 can be routed to the **Result** signal by the ResultSrc multiplexer. Only the ALU output needs to be routed to the PCTarget signal. So, we add a control signal (**PCTargetSrc**) and a multiplexer to select the correct PCTarget (either from the ALU or the PC-relative adder).

Enhanced datapath to support jalr

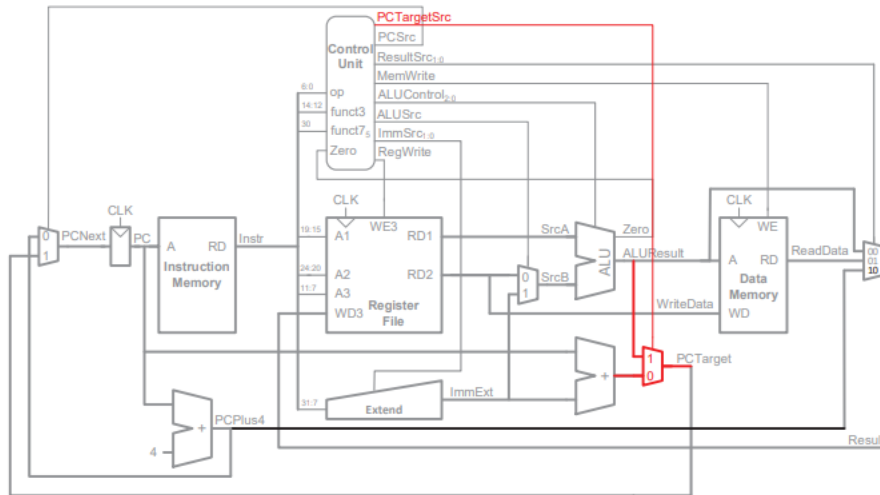

Main Decoder enhanced to support jalr

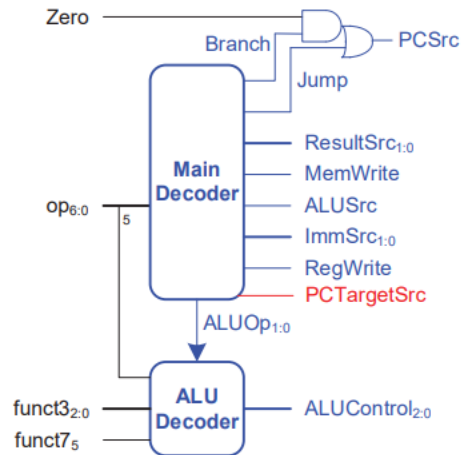

Main Decoder truth table enhanced to support jalr

Instruction	Opcode	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump	PCTargetSrc
lw	0000011	1	000	1	0	01	0	00	0	x
sw	0100011	0	001	1	1	xx	0	00	0	x
R-type	0110011	1	xxx	0	0	00	0	10	0	x
beq	1100011	0	010	0	0	xx	1	01	0	0


I-type ALU	0010011	1	000	0	0	00	0	10	0	x
jal	1101111	1	011	x	0	10	0	xx	1	0
jalr	1100111	1	000	1	0	10	0	xx	1	1

(j) sb


We add a WriteData Unit (WD Unit) to the datapath to write either RD2 or RD2 bit-swizzled with ReadData for sub-word writes. For sb, the least significant byte (lsb) of

RD2 (**rs2**'s contents), replaces a byte of data in the *ReadData* bus depending on the byte offset of the memory address, $ALUResult_{1:0}$. We add a *StoreType* output to the control unit to choose either the entire word or the bit-swizzled word to write to memory. The updated figures and additional hardware is shown below.

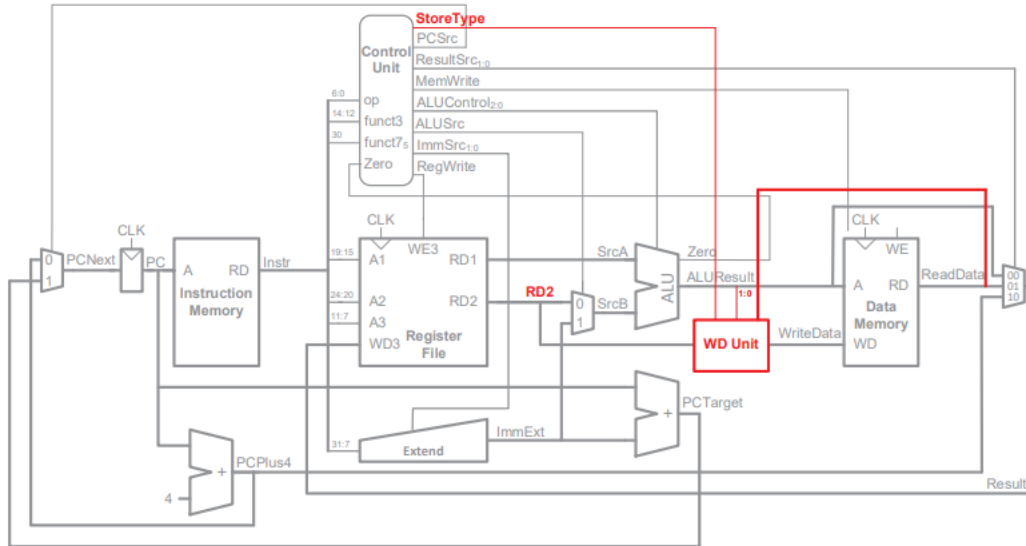Enhanced datapath to support sb (WD Unit shown in next figure)



WD Unit

 


WD Unit

Main Decoder truth table enhanced to support sb

Instruction	Opcode	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
lw	0000011	1	000	1	0	01	0	00	0
sw / sb	0100011	0	001	1	1	xx	0	00	0
R-type	0110011	1	xxx	0	0	xx	0	10	0
beq	1100011	0	010	0	0	xx	1	01	0
I-type ALU	0010011	1	000	0	0	00	0	10	0
jal	1101111	1	011	x	0	10	0	xx	1

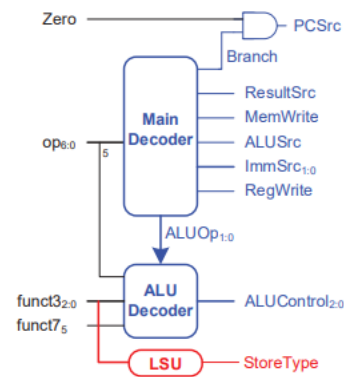Enhanced control unit for **sb** : added Load/Store Unit (LSU)



Load/Store Unit (LSU) truth table to support **sb**

funct3	StoreType	Instruction
000	1	sb
010	0	sw