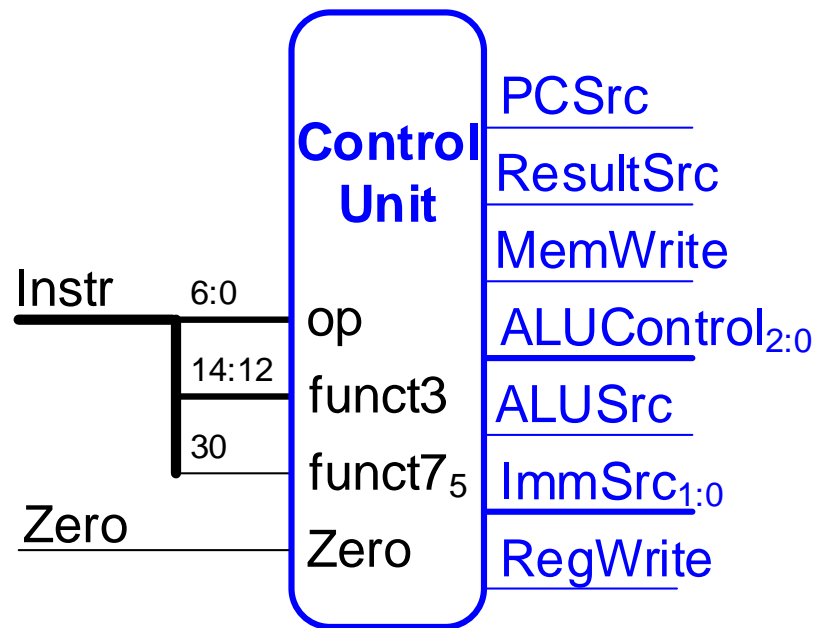


Chapter 7: Microarchitecture


Single-Cycle Control

Single-Cycle Control

High-Level View




Low-Level View

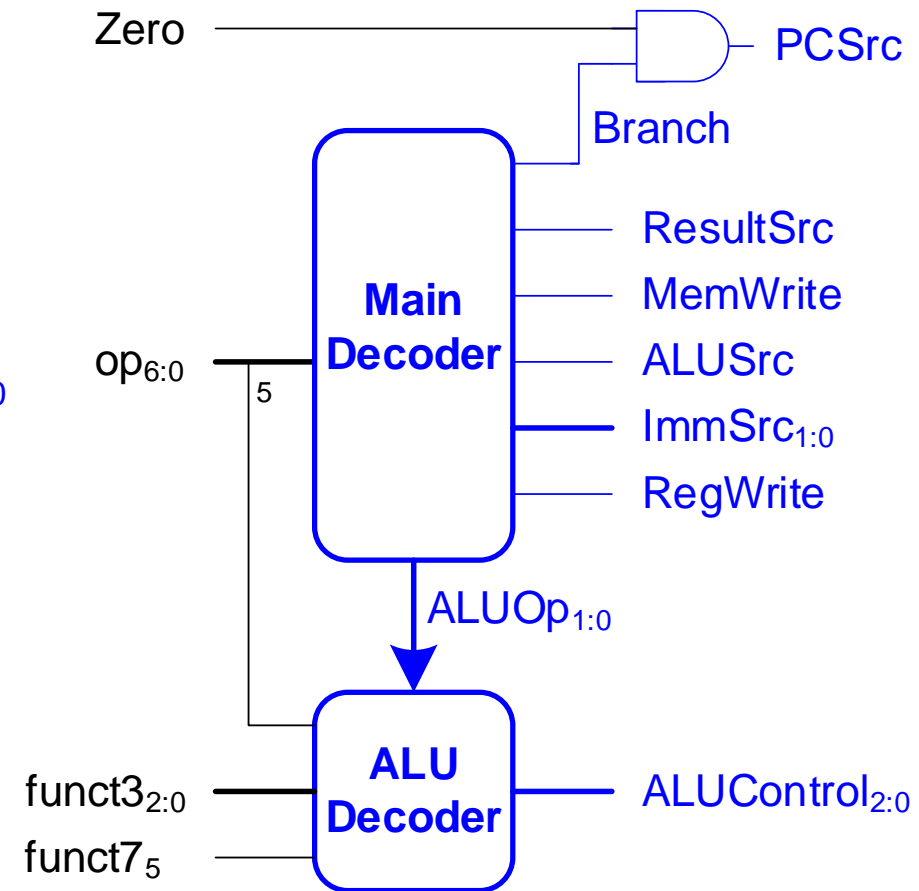


Single-Cycle Control: Main Decoder

op	Instr.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw							
35	sw							
51	R-type							
99	beq							

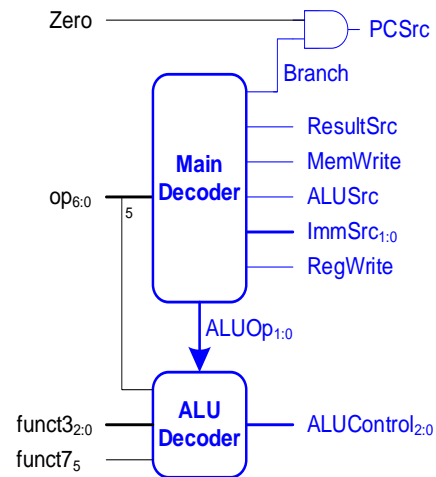


Review: ALU

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

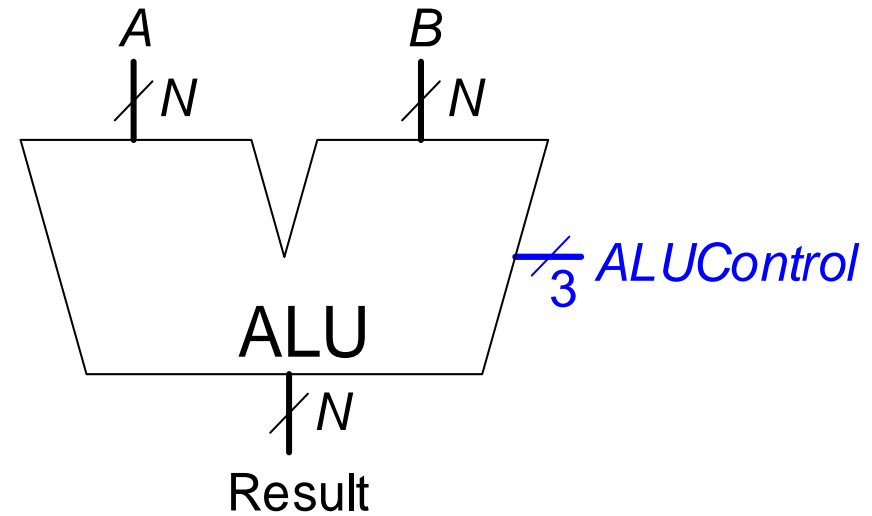


Review: ALU

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

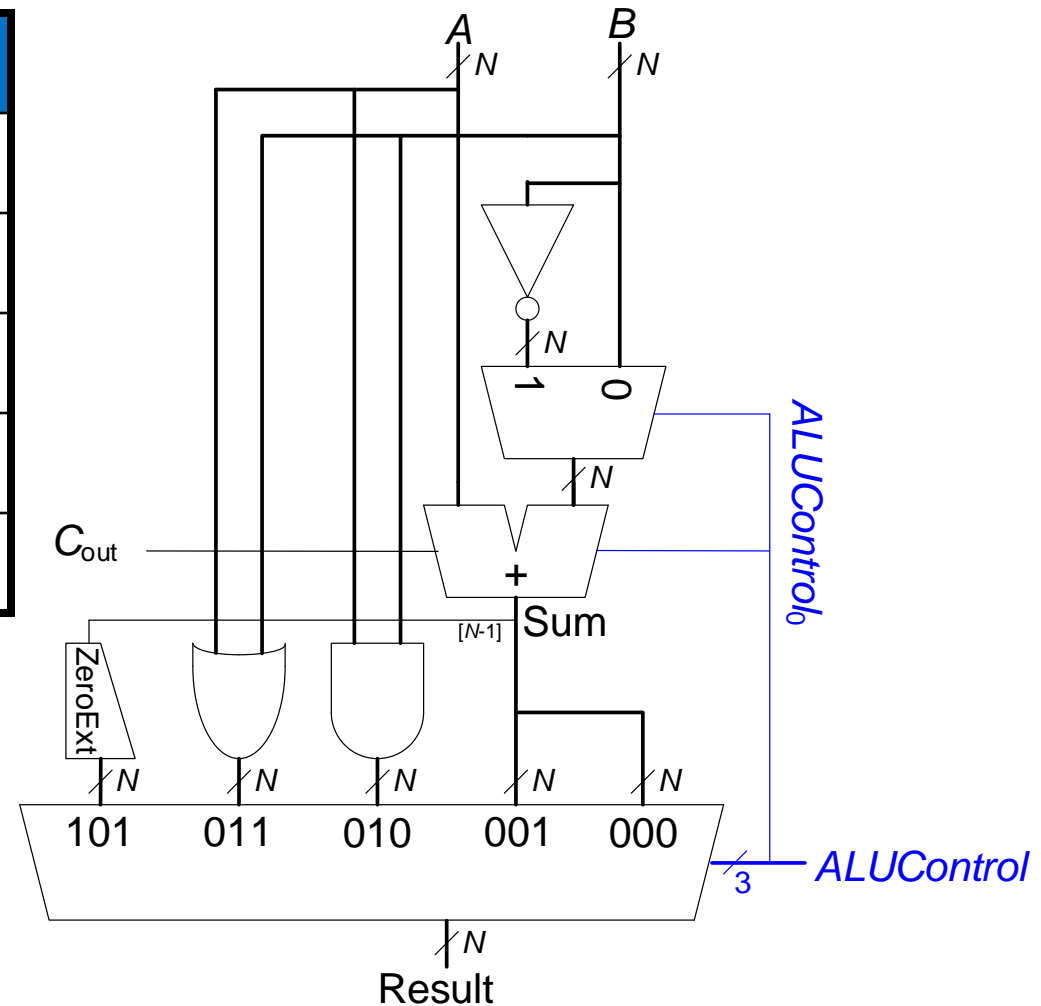


Single-Cycle Control: ALU Decoder

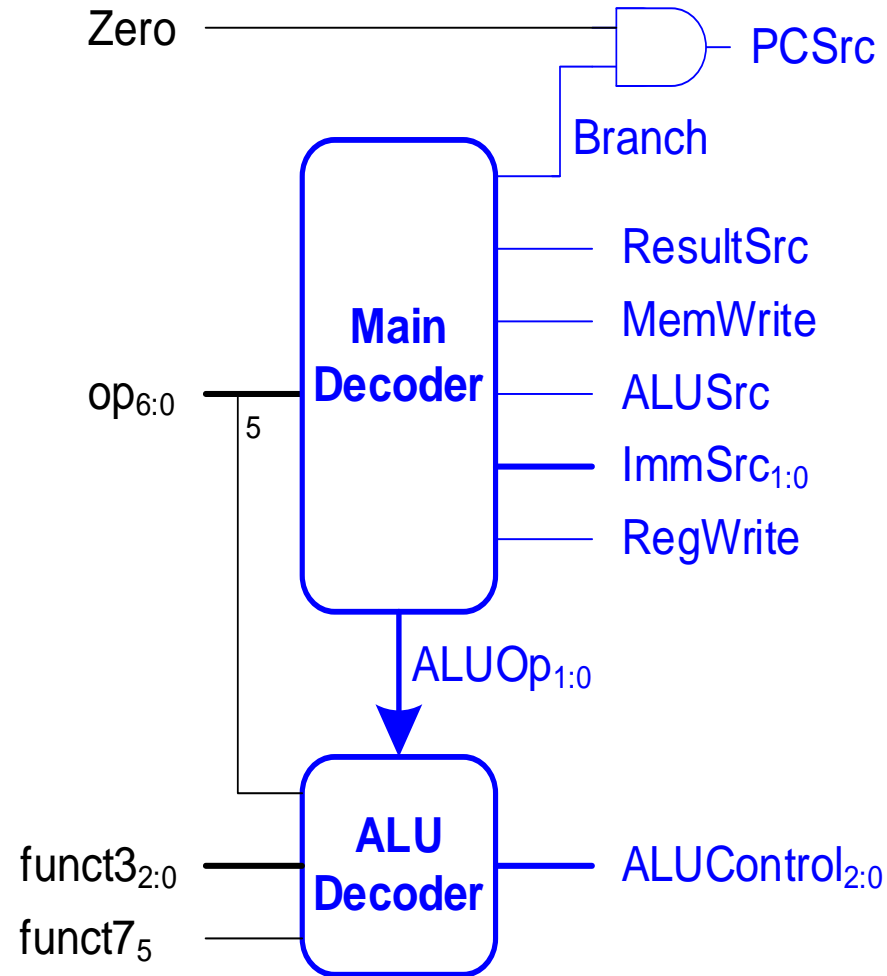


Single-Cycle Control: ALU Decoder

$ALUOp$	funct3	$op_5, funct7_5$	Instruction	$ALUControl_{2:0}$
00	x	x	lw, sw	000 (add)
01	x	x	beq	001 (subtract)
10	000	00, 01, 10	add	000 (add)
	000	11	sub	001 (subtract)
	010	x	slt	101 (set less than)
	110	x	or	011 (or)
	111	x	and	010 (and)

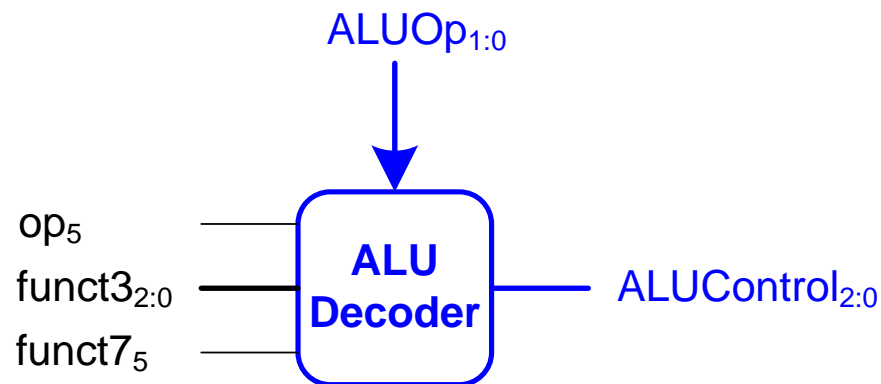

Example: and

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
51	R-type	1	XX	0	0	0	0	10

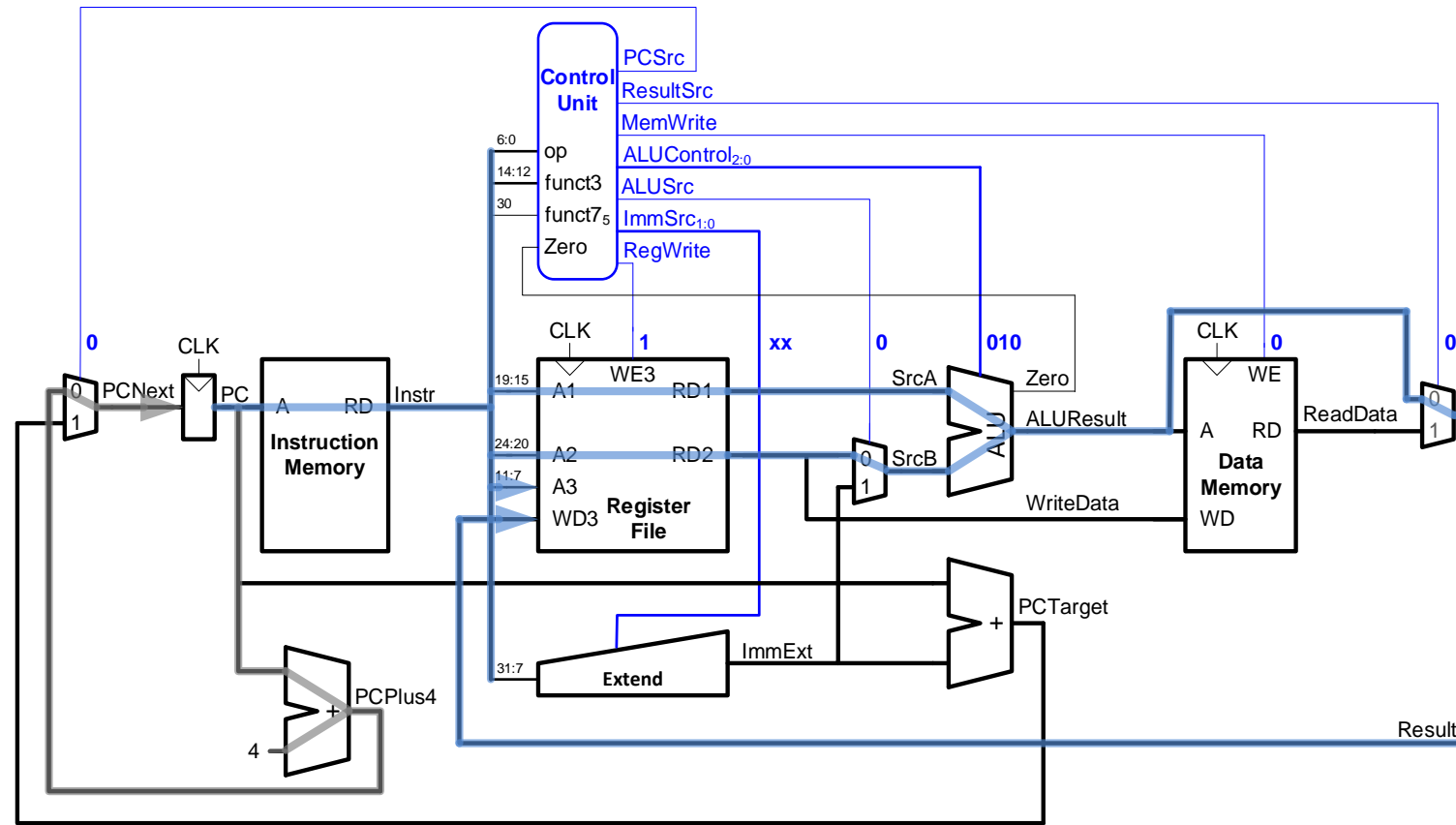

and x5, x6, x7