

Chapter 7: Microarchitecture

Multicycle Performance

Multicycle Processor Performance


- Instructions take different number of cycles:
 - 3 cycles: `beq`
 - 4 cycles: `R-type`, `addi`, `sw`, `jal`
 - 5 cycles: `lw`
- CPI is weighted average
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 13% branches
 - 52% R-type

$$\text{Average CPI} = (0.13)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$$

Multicycle Critical Path

Potential Critical Paths:

- Calculate PC + 4 or
- Read Memory

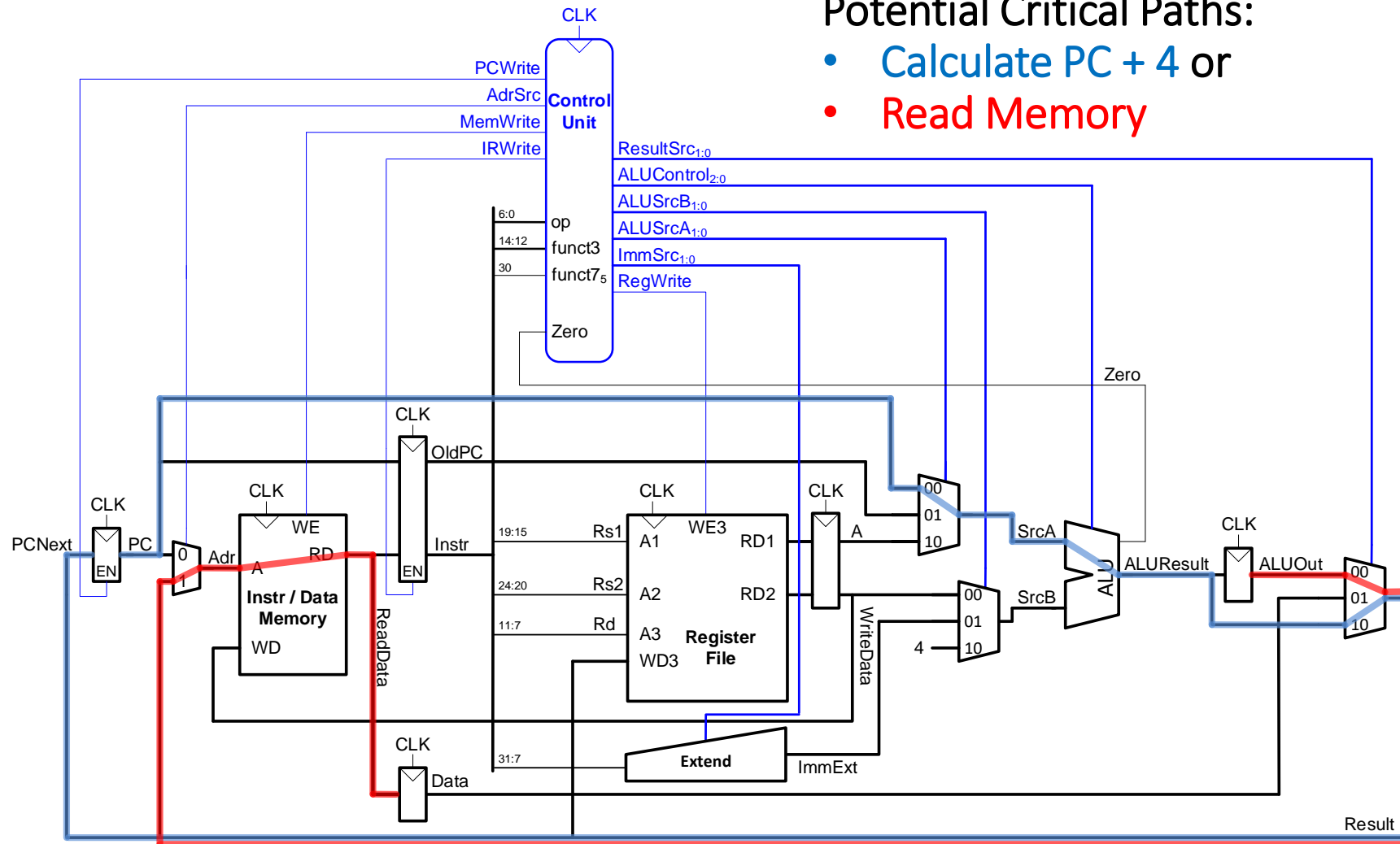

Multicycle Processor Performance

Multicycle critical path:

- **Assumptions:**
 - RF is faster than memory
 - Writing memory is faster than reading memory

$$T_{c_multi} = t_{pcq} + t_{dec} + 2t_{mux} + \max(t_{ALU}, t_{mem}) + t_{setup}$$

Multicycle Performance Example

| Element | Parameter | Delay (ps) |
|------------------------|---------------|------------|
| Register clock-to-Q | t_{pcq_PC} | 40 |
| Register setup | t_{setup} | 50 |
| Multiplexer | t_{mux} | 30 |
| AND-OR gate | t_{AND-OR} | 20 |
| ALU | t_{ALU} | 120 |
| Decoder (Control Unit) | t_{dec} | 25 |
| Extend unit | t_{dec} | 35 |
| Memory read | t_{mem} | 200 |
| Register file read | t_{RFread} | 100 |
| Register file setup | $t_{RFsetup}$ | 60 |

$$T_{c_multi} = t_{pcq} + t_{dec} + 2t_{mux} + \max(t_{ALU}, t_{mem}) + t_{setup}$$
$$=$$

Multicycle Performance Example

For a program with **100 billion** instructions executing on a **multicycle** RISC-V processor

- **CPI** = 4.12 cycles/instruction
- **Clock cycle time:** $T_{c_multi} = 375 \text{ ps}$

$$\text{Execution Time} = (\# \text{ instructions}) \times \text{CPI} \times T_c$$

Chapter 7: Microarchitecture


Pipelined RISC-V Processor

Pipelined RISC-V Processor


- Temporal parallelism
- Divide single-cycle processor into 5 stages:
 - Fetch
 - Decode
 - Execute
 - Memory
 - Writeback
- Add **pipeline registers** between stages

Single-Cycle vs. Pipelined Processor


Single-Cycle

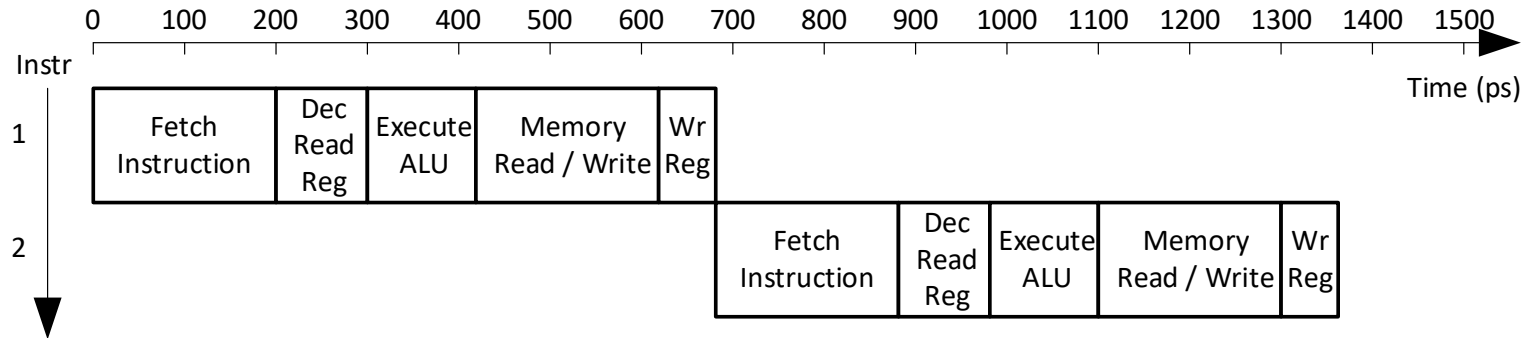


Pipelined

 


Pipelined Processor Abstraction

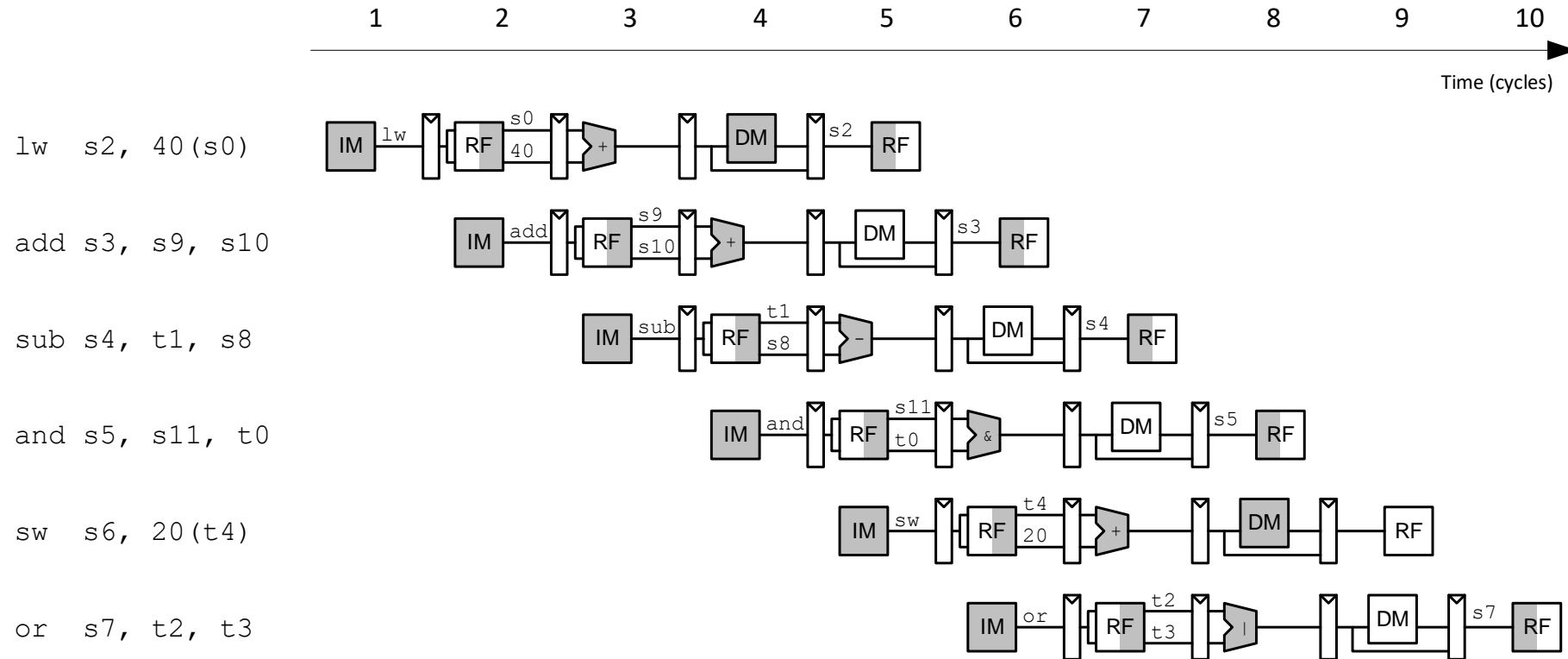


Single-Cycle & Pipelined Datapaths

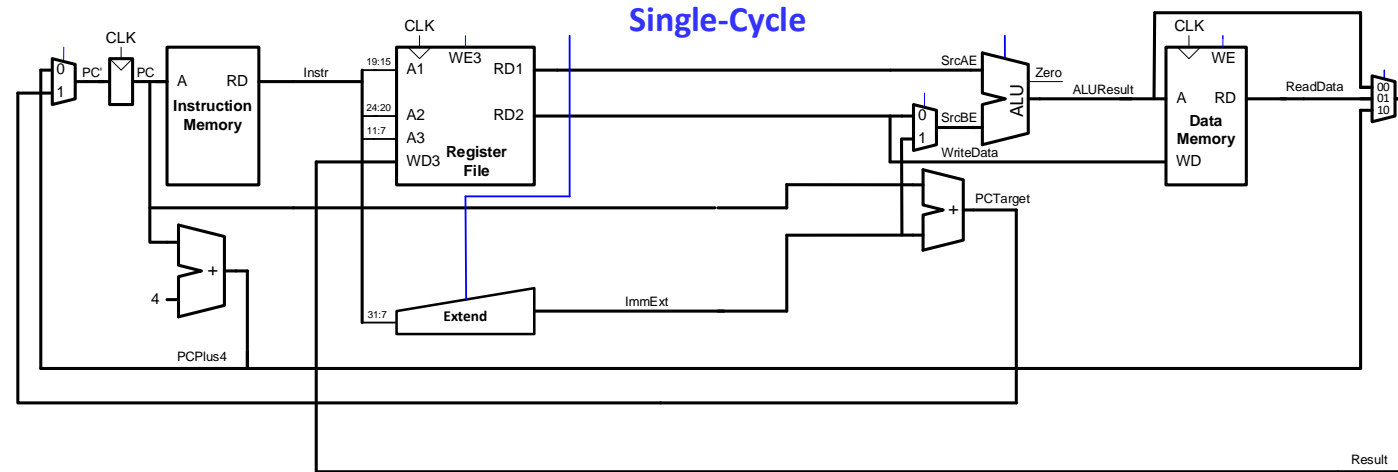

 Signals in Pipelined Processor are appended with first letter of stage (i.e., PC_F, PC_D, PC_E).




Corrected Pipelined Datapath

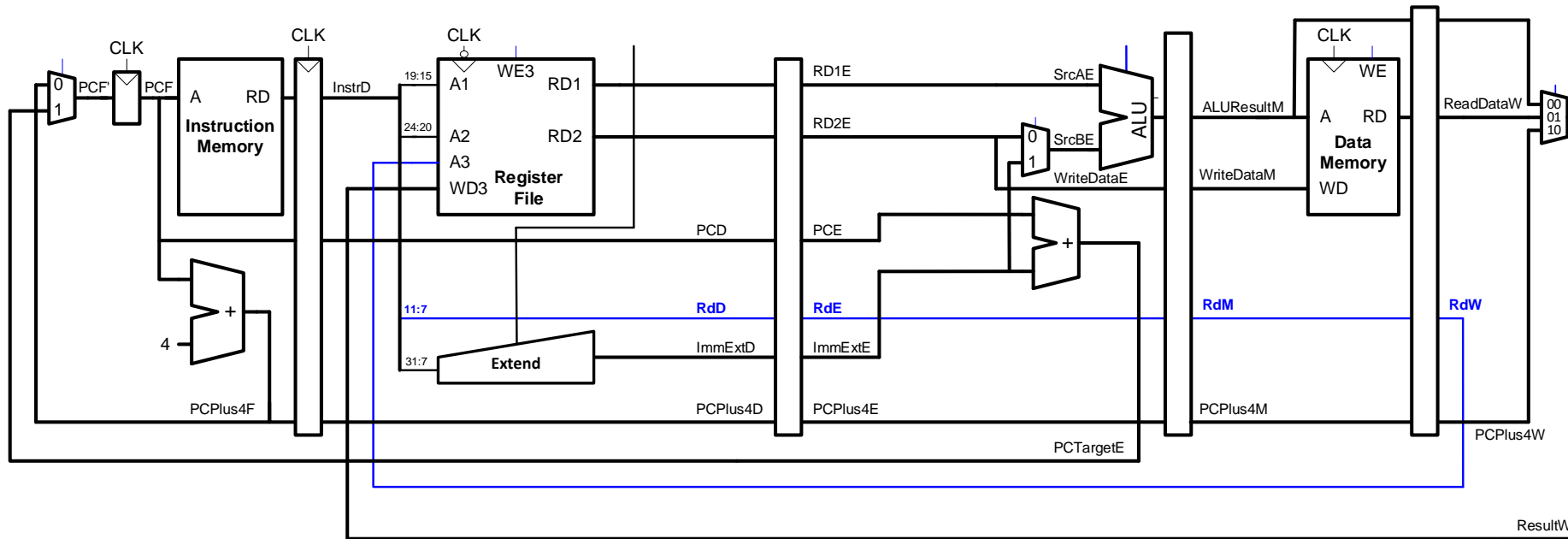

- *Rd* must arrive at same time as *Result*
- Register file written on **falling edge** of *CLK*

Pipelined Processor with Control

 

- **Same control unit** as single-cycle processor
- **Control signals travel with** the instruction (drop off when used)