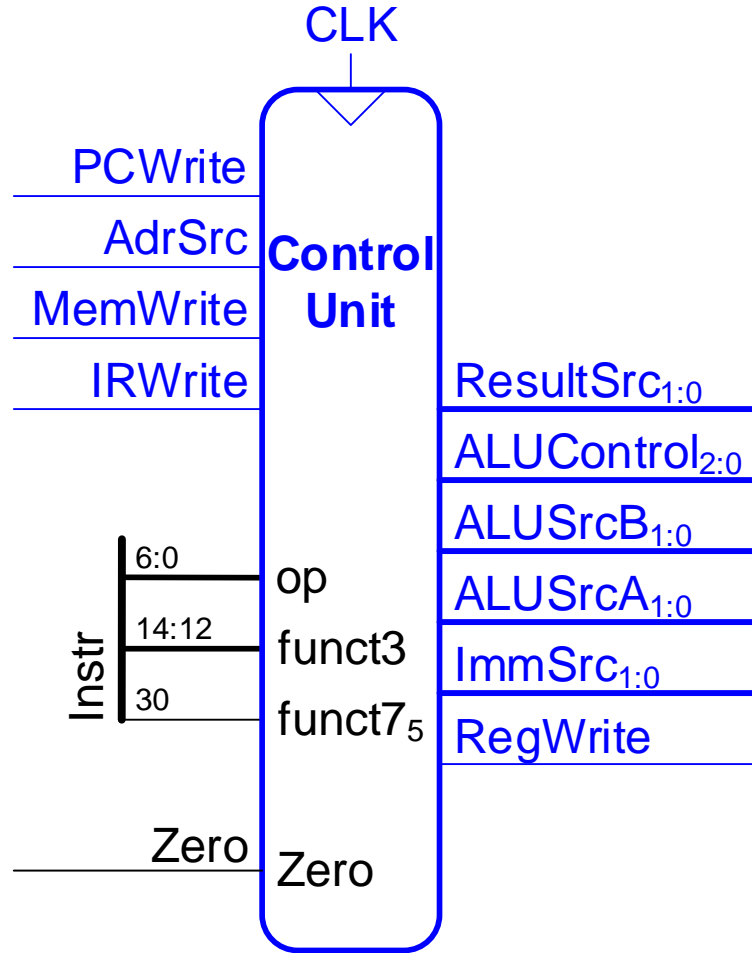


Chapter 7: Microarchitecture


Multicycle Control

Multicycle Control


High-Level View



Low-Level View

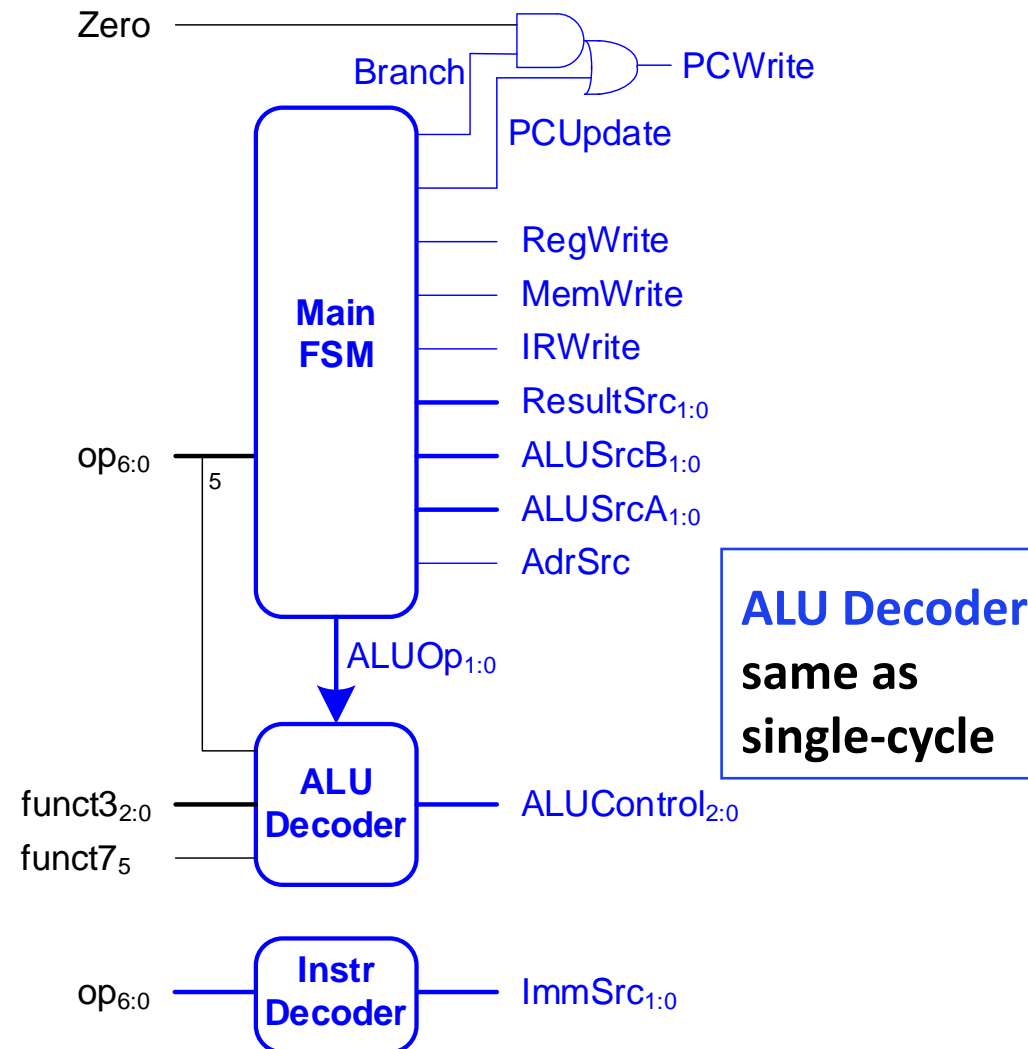


Multicycle Control: Instruction Decoder

 

op	Instruction	ImmSrc
3	lw	00
35	sw	01
51	R-type	XX
99	beq	10


Multicycle Control: Main FSM

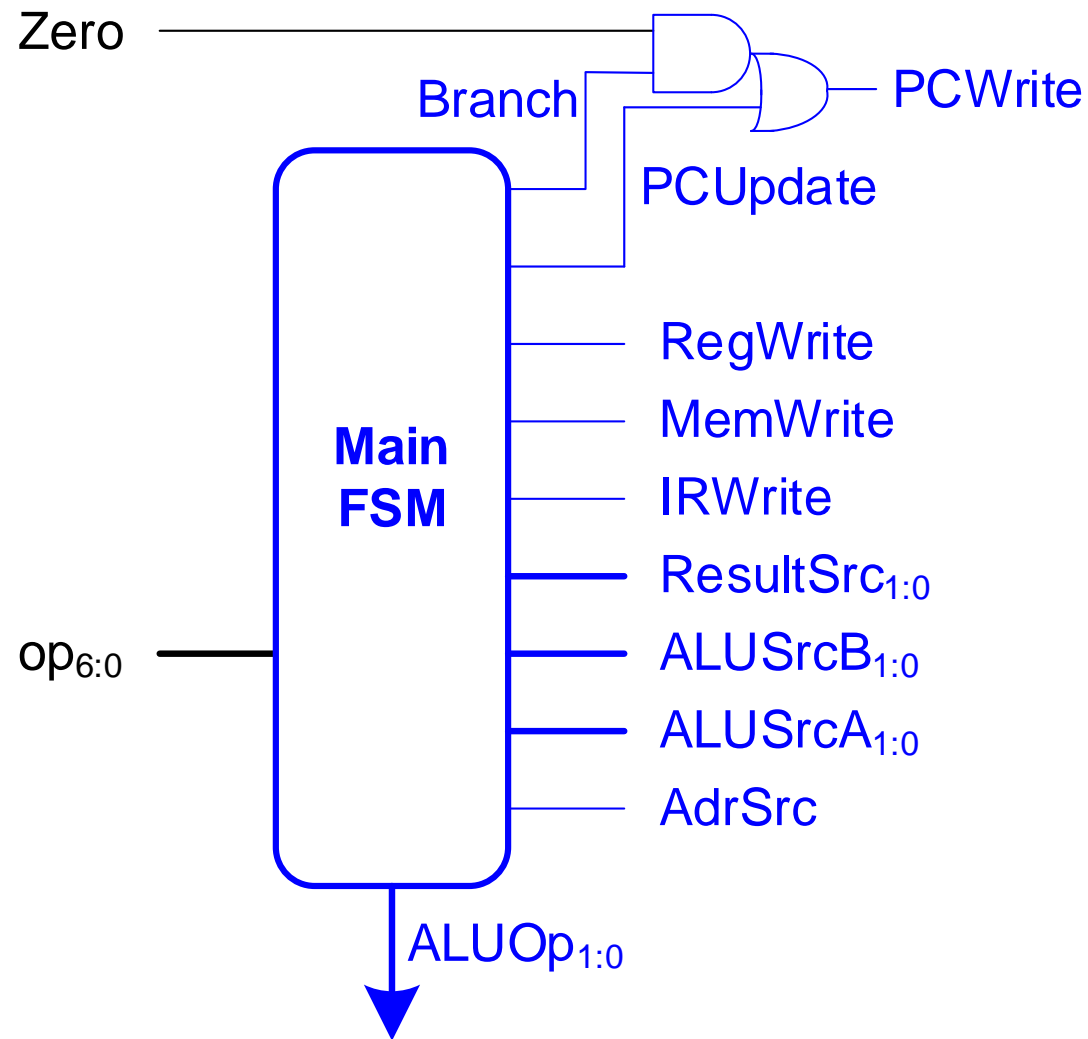


To declutter FSM:

- **Write enable signals** (RegWrite, MemWrite, IRWrite, PCUpdate, and Branch) are **0** if not listed in a state.
- **Other signals are don't care** if not listed in a state


Main FSM: Fetch

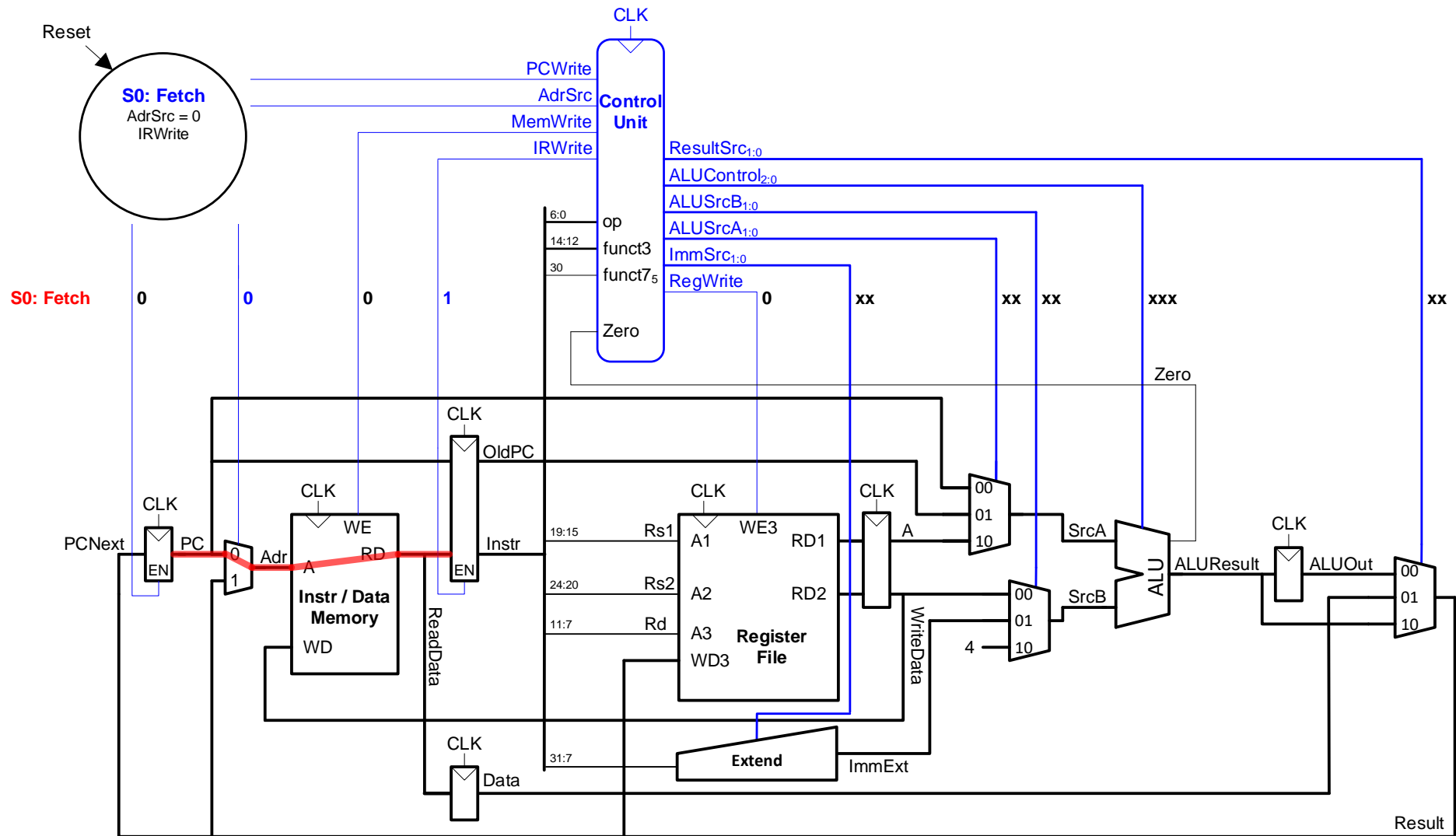


Main FSM: Decode

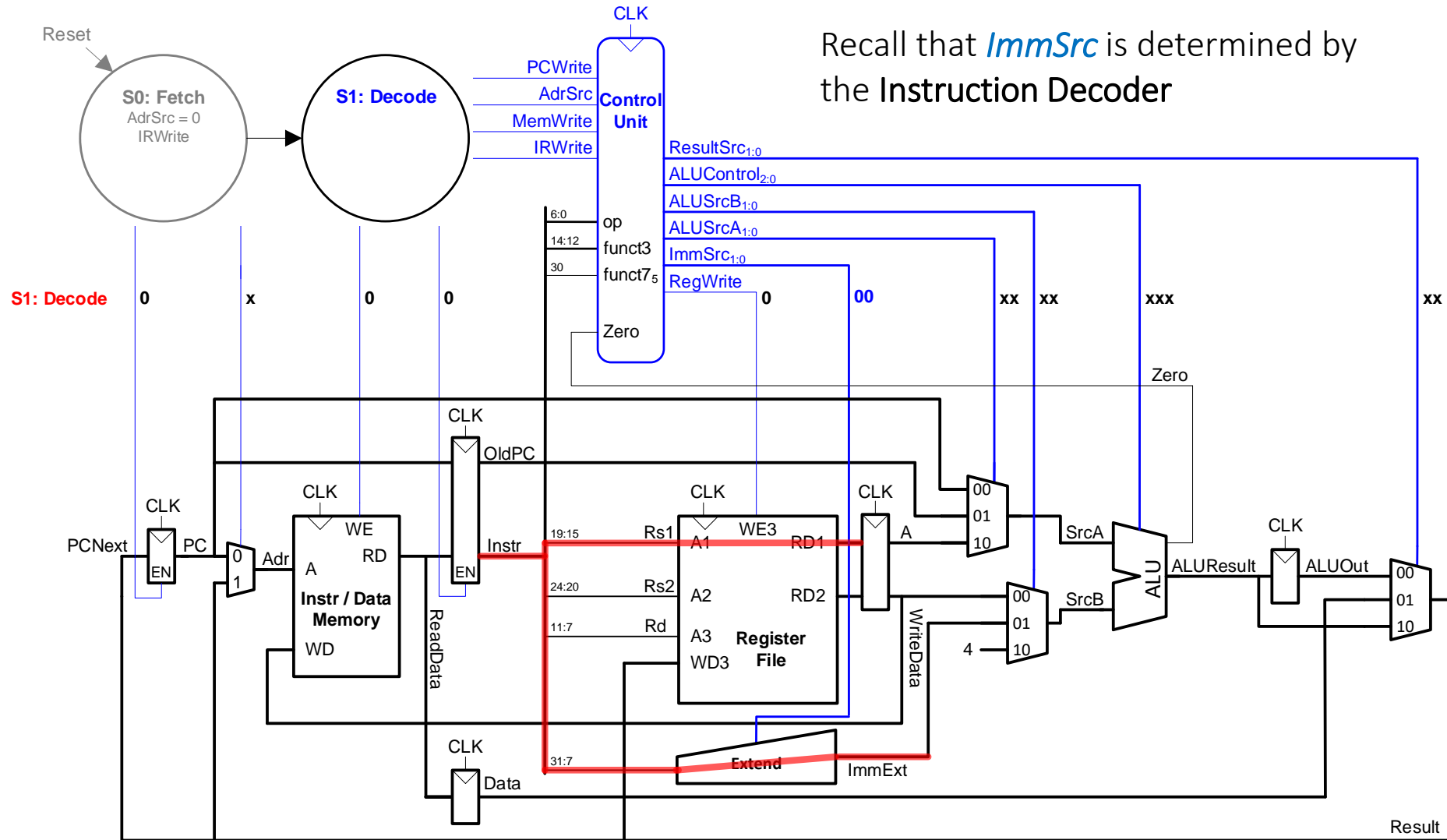


Main FSM: Address

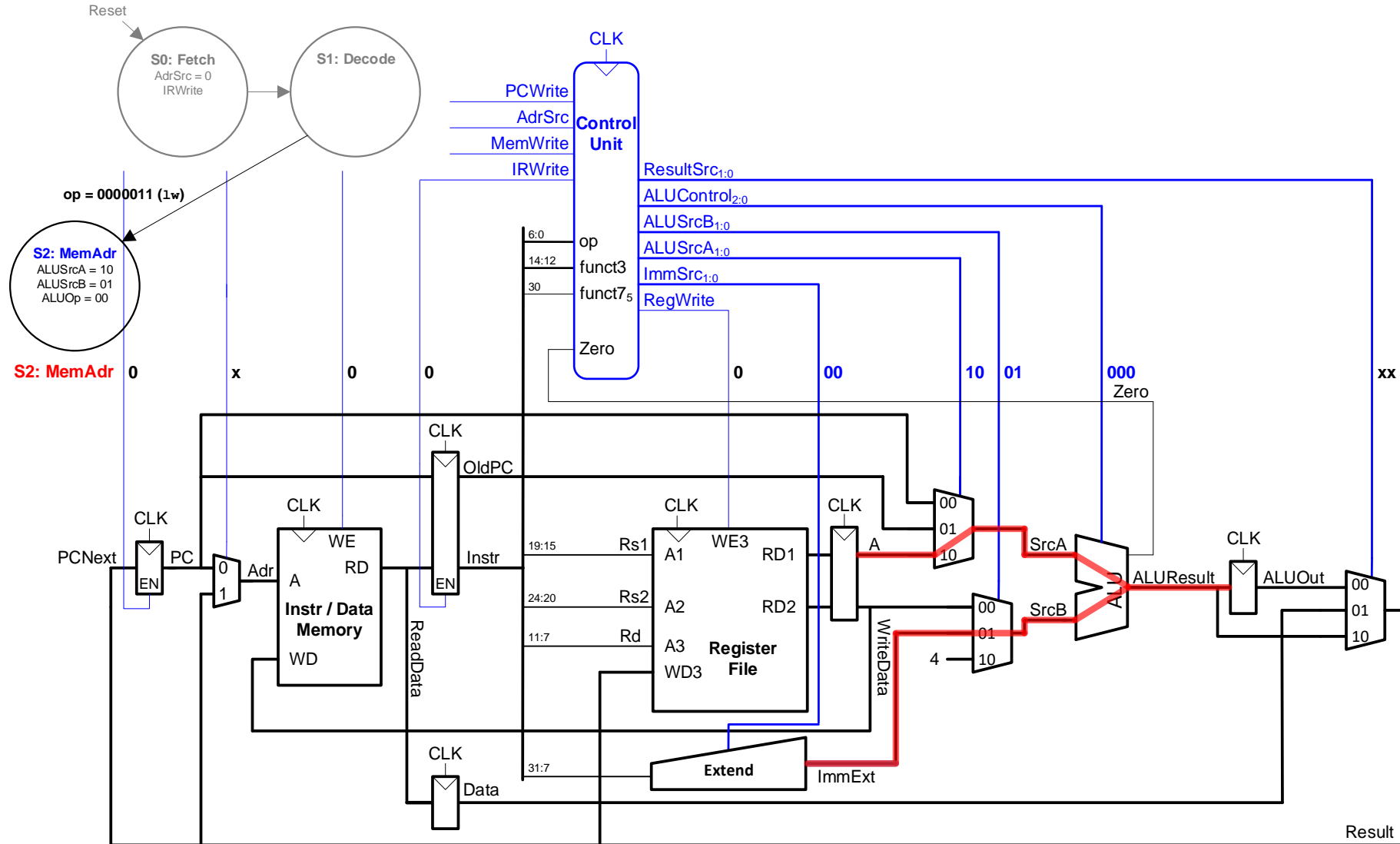


Main FSM: Read Memory

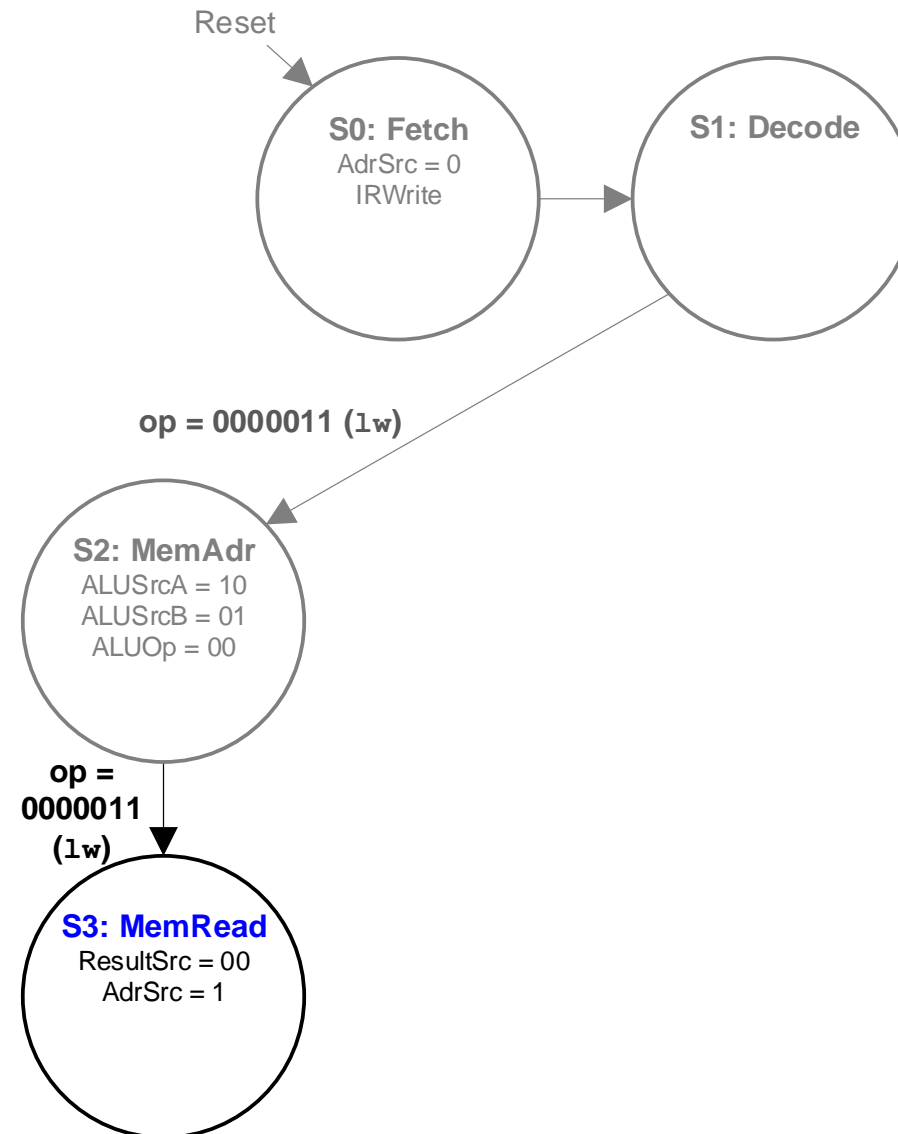


Main FSM: Read Memory Datapath

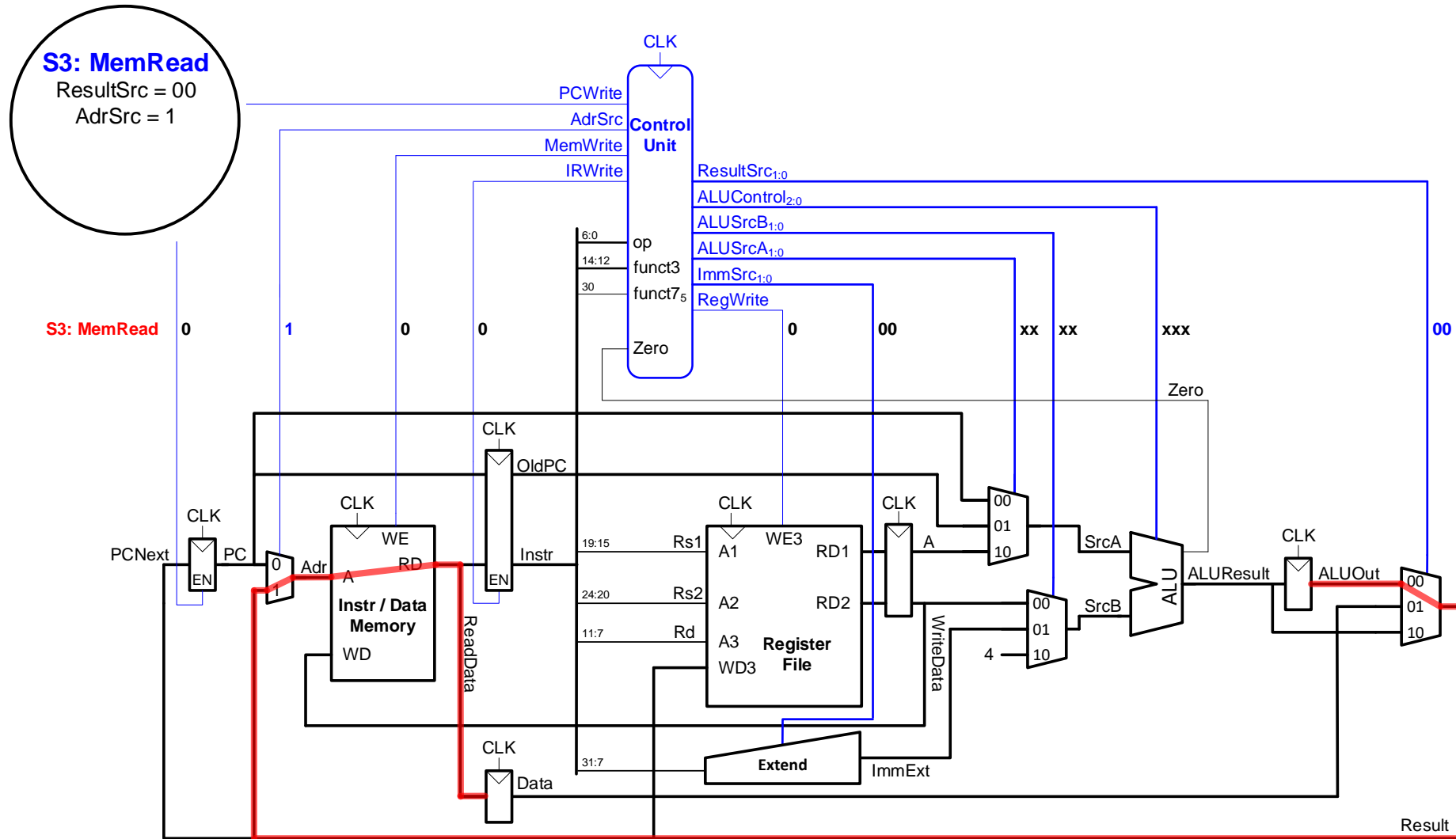

Main FSM: Write RF

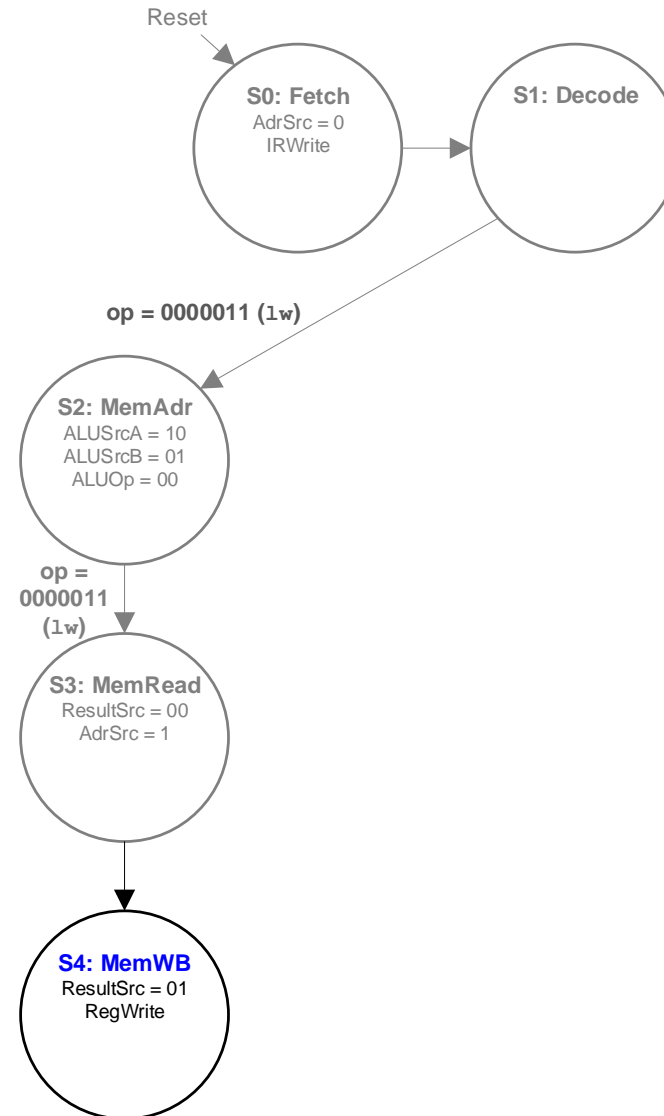


Main FSM: Write RF Datapath

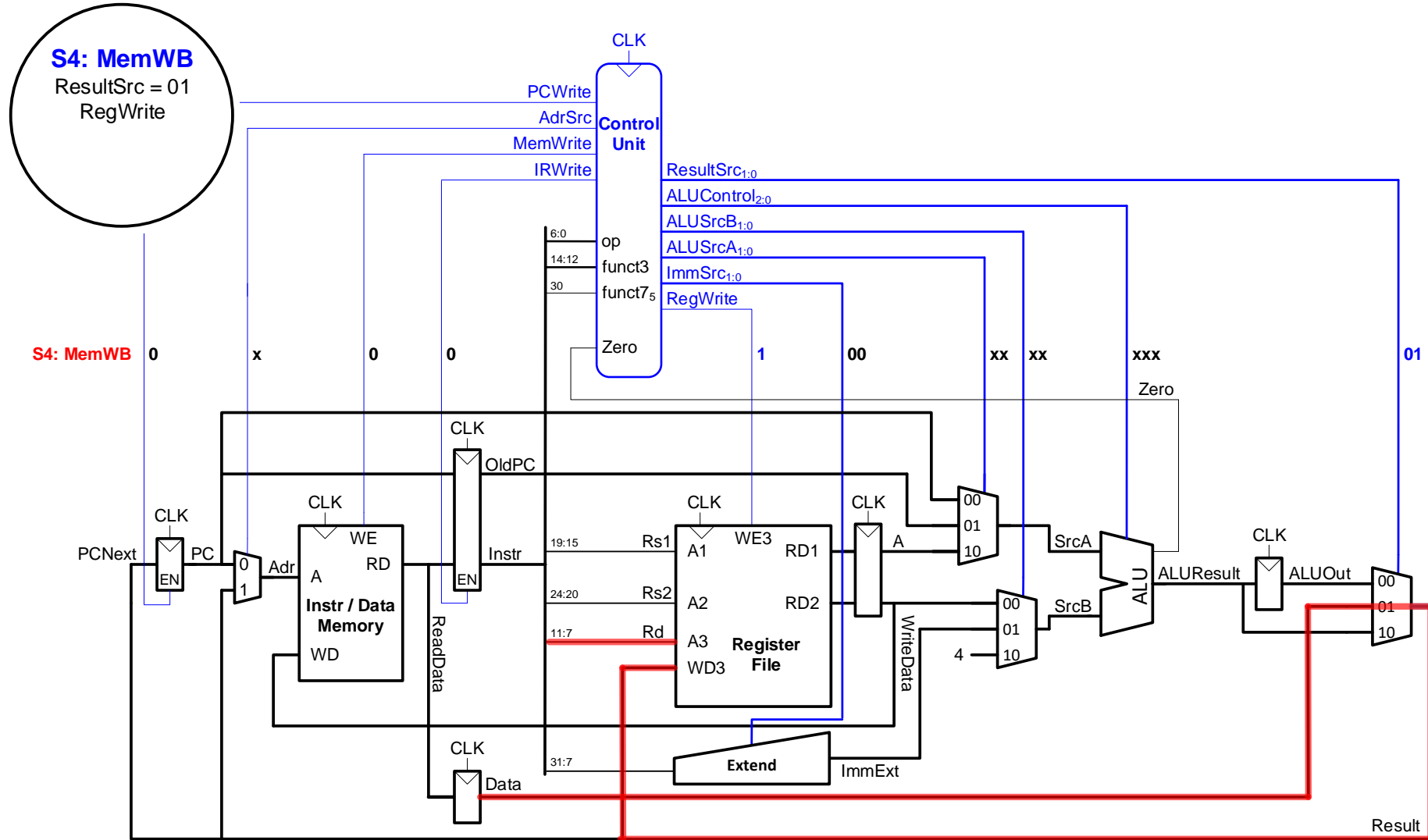


Main FSM: Fetch Revisited

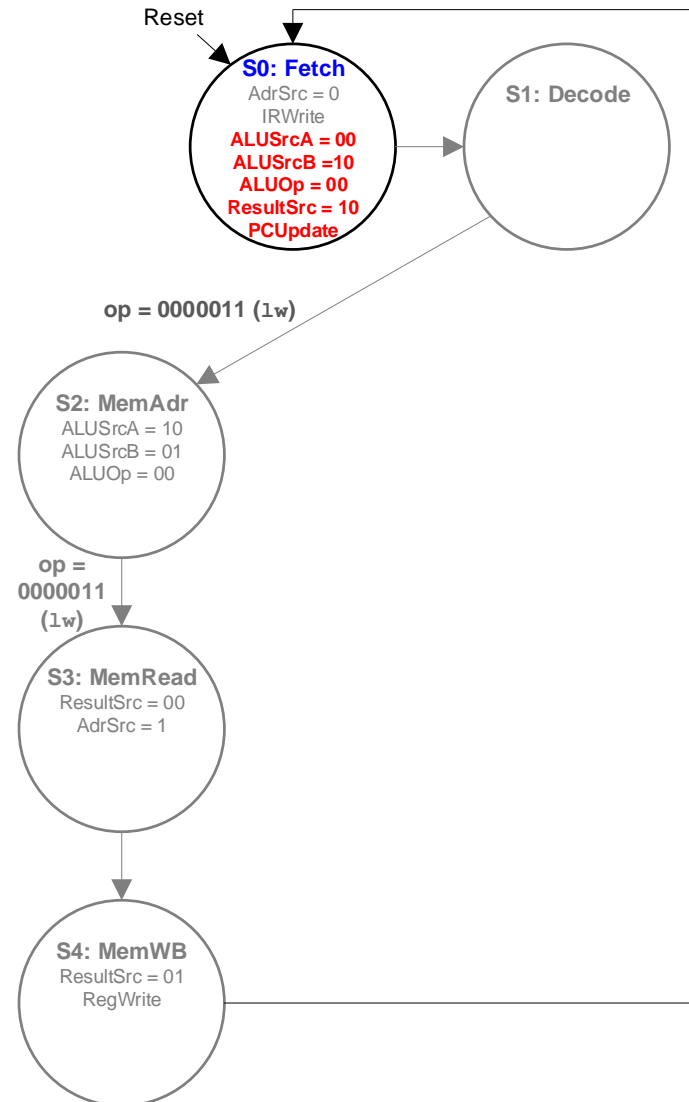Calculate **PC+4**
during Fetch stage
(ALU isn't being
used)




Main FSM: Fetch (PC+4) Datapath

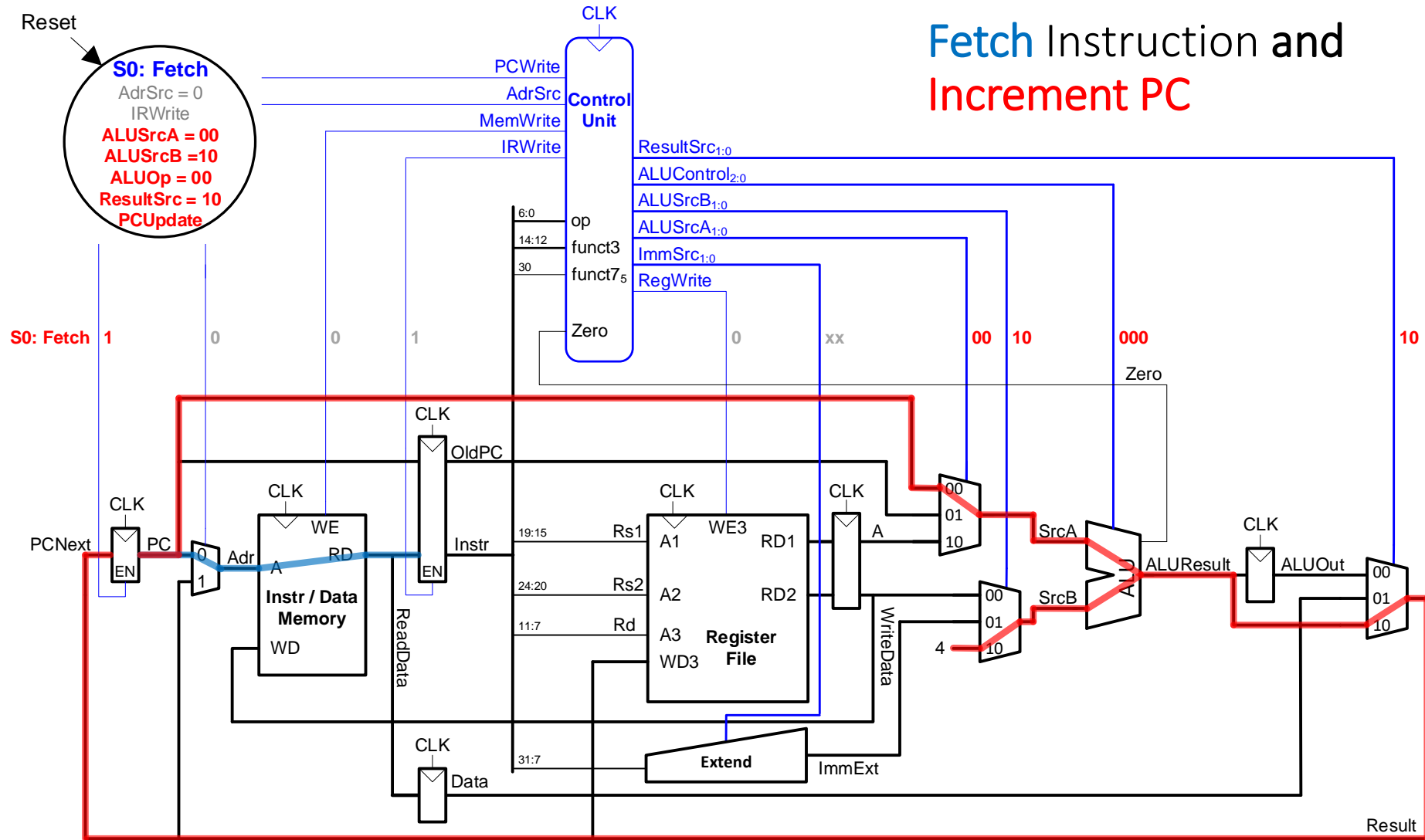


Chapter 7: Microarchitecture

Multicycle Control: Other Instructions


Main FSM: sw

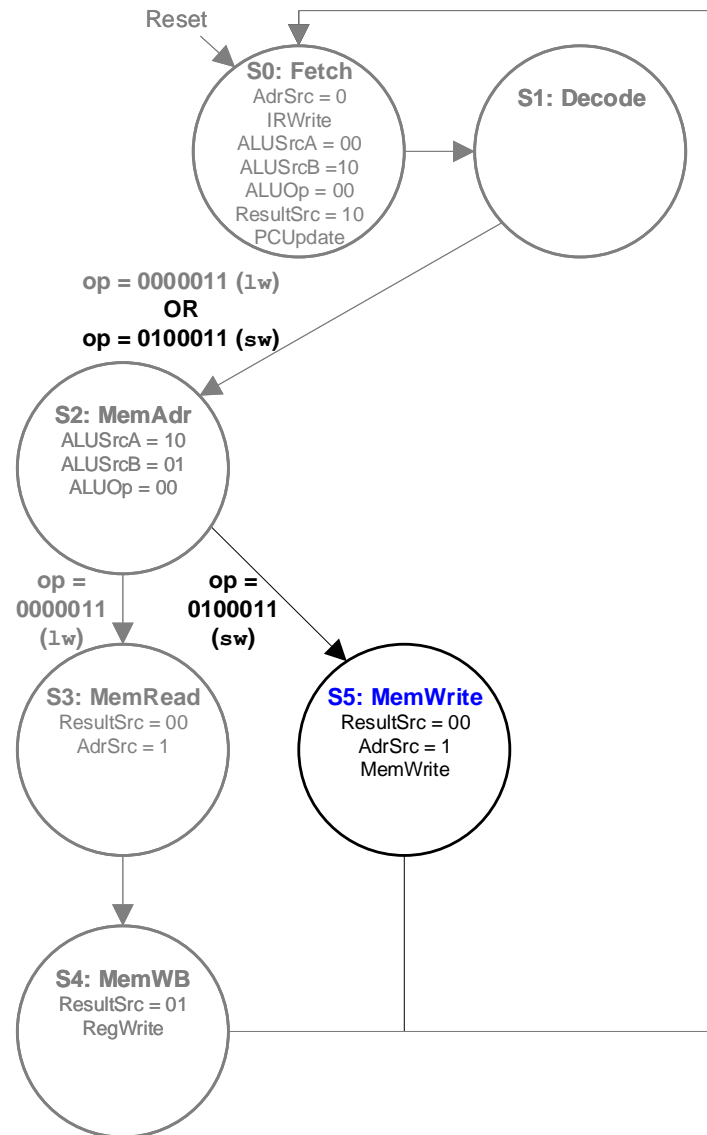


Main FSM: sw Datapath

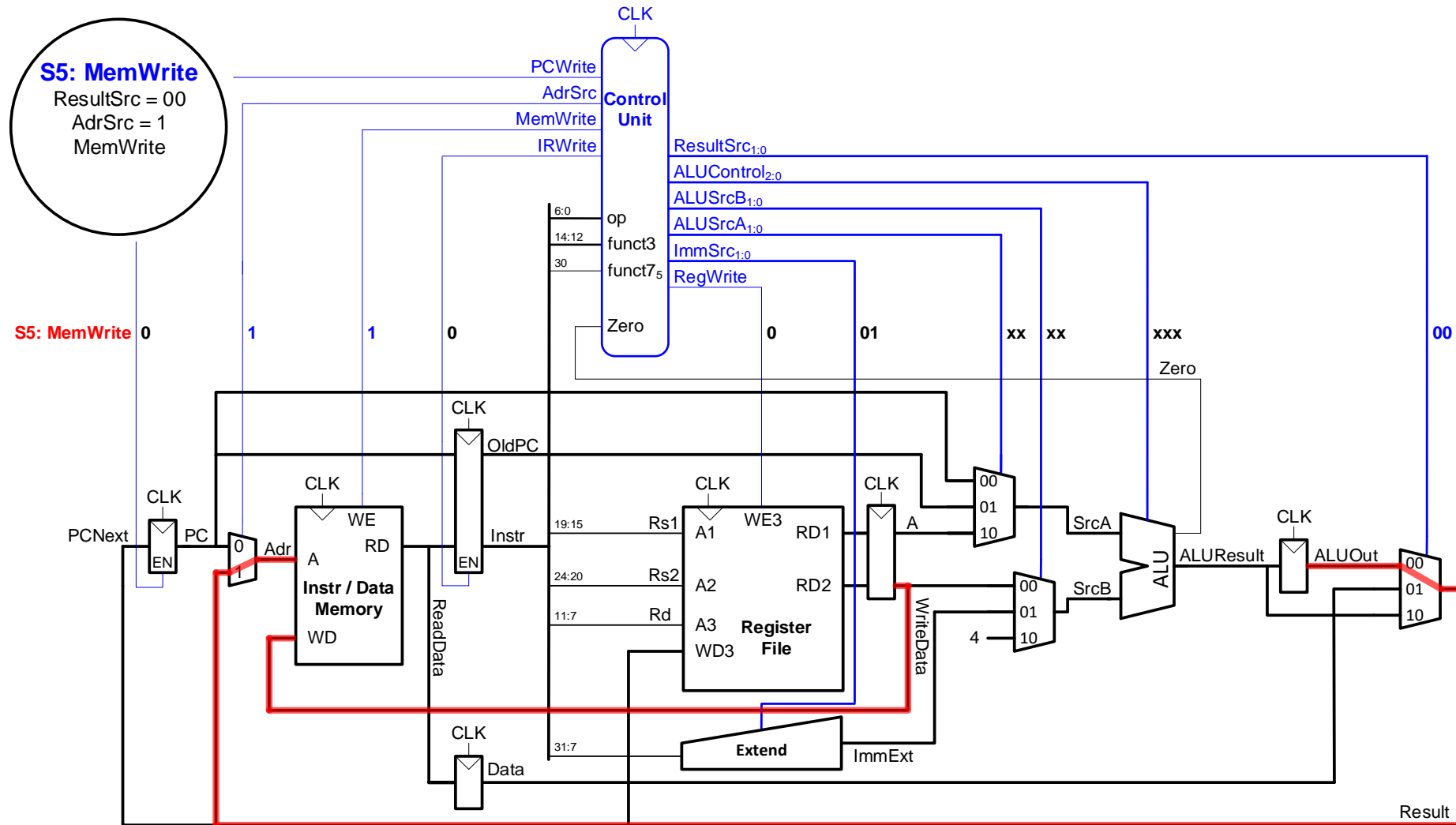


Main FSM: R-Type Execute

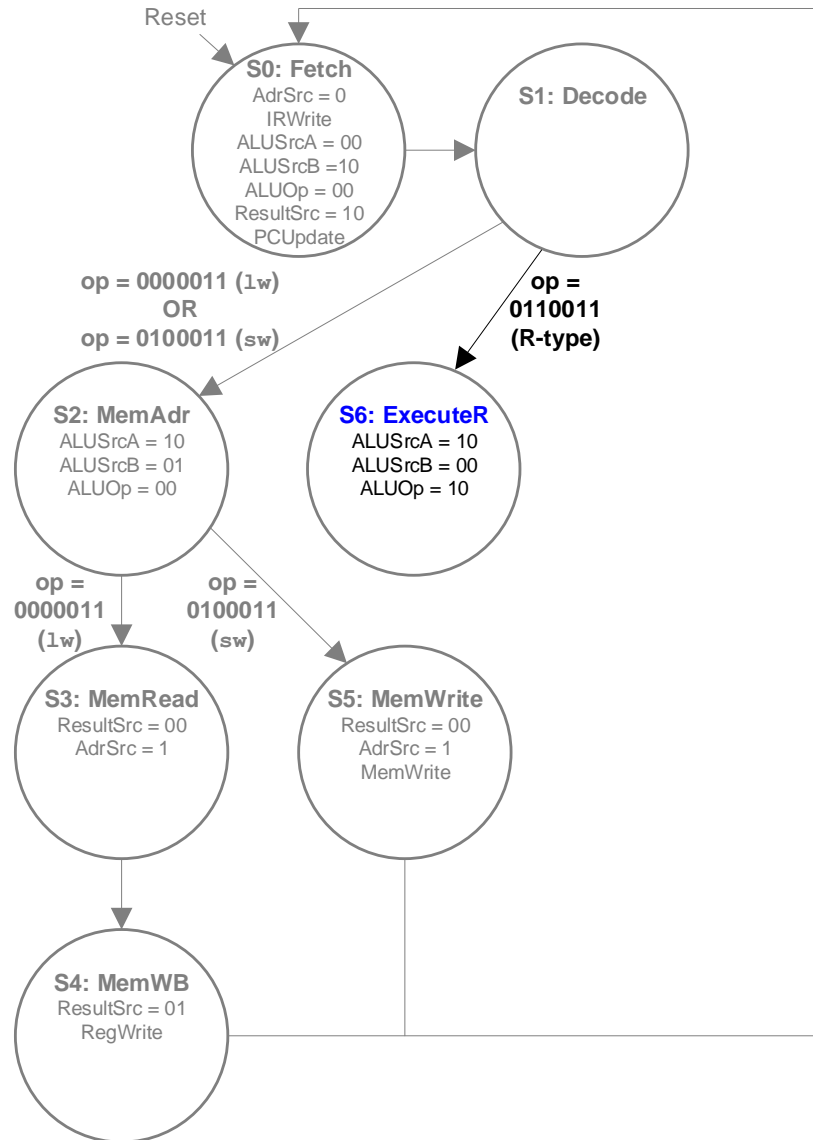


Main FSM: R-Type Execute Datapath

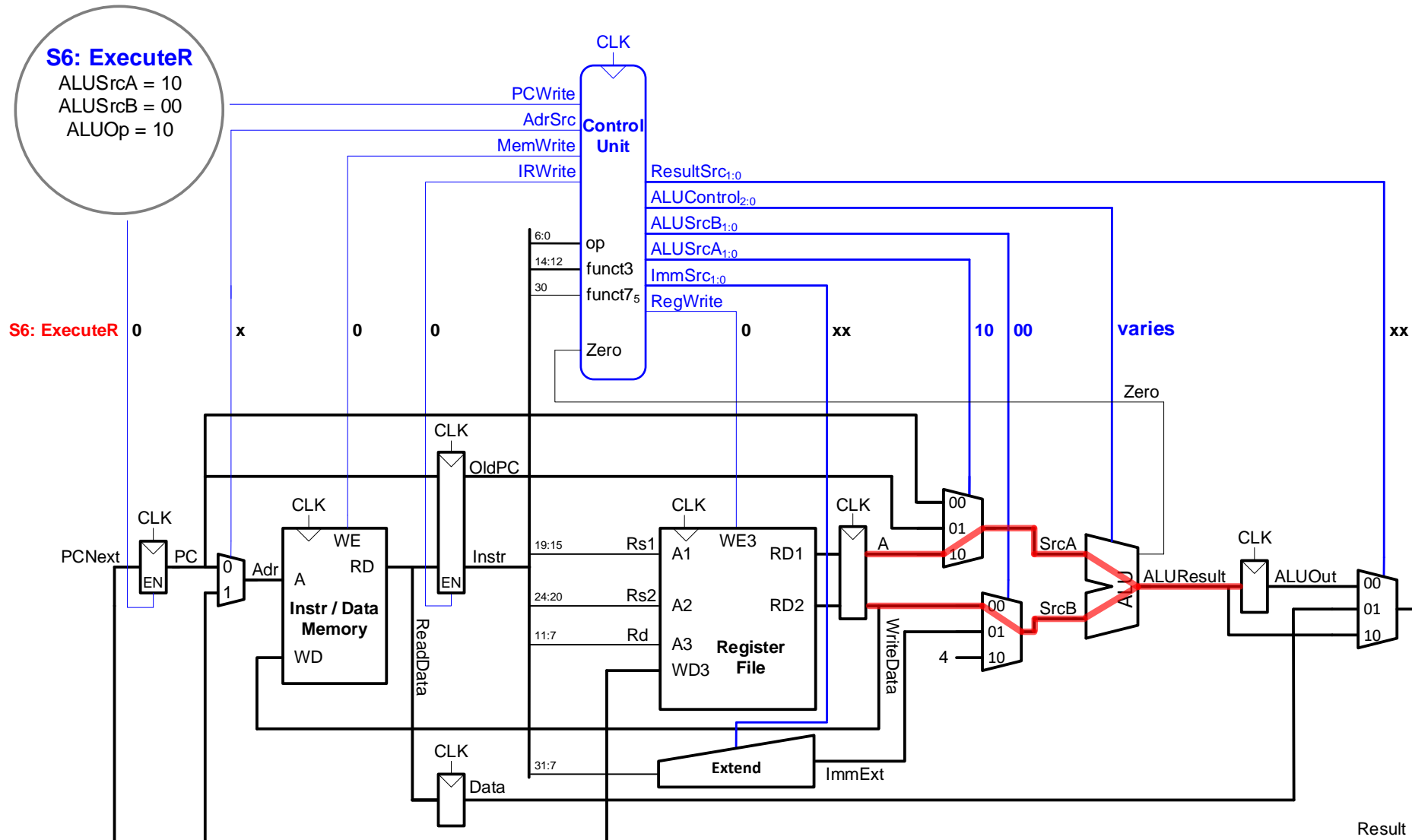

Main FSM: R-Type ALU Write Back

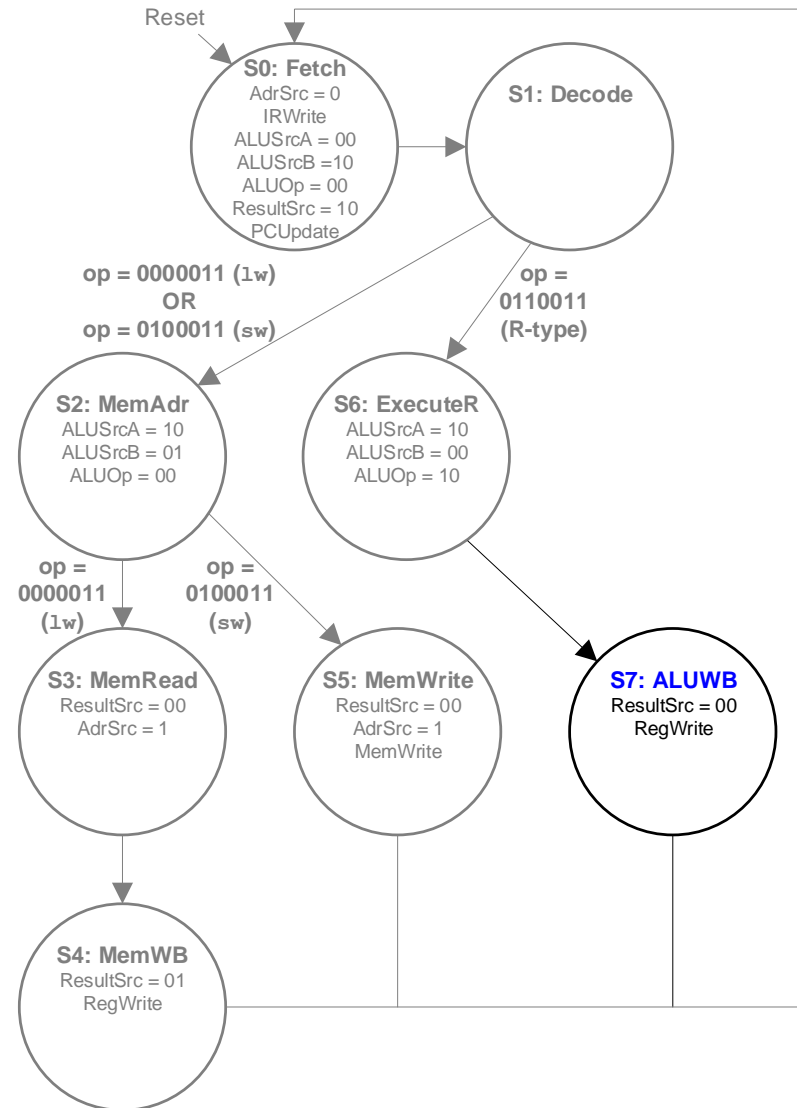


Main FSM: R-Type ALU Write Back

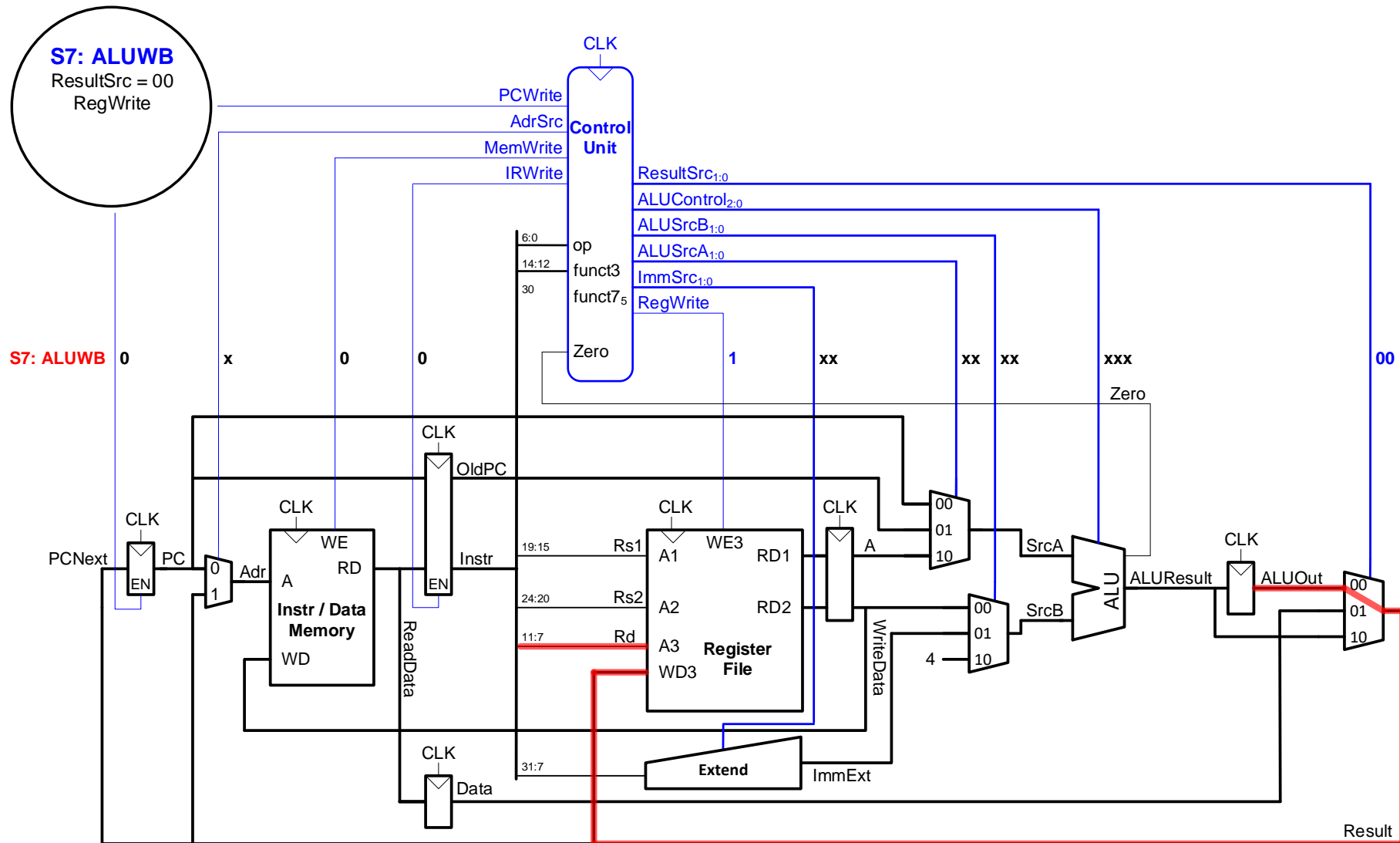


Main FSM: beq

- **Need to calculate:**
 - Branch Target Address
 - **rs1** - **rs2** (to see if equal)
- **ALU** isn't being used in Decode stage
 - Use it to calculate Target Address ($PC + imm$)


Main FSM: Decode Revisited

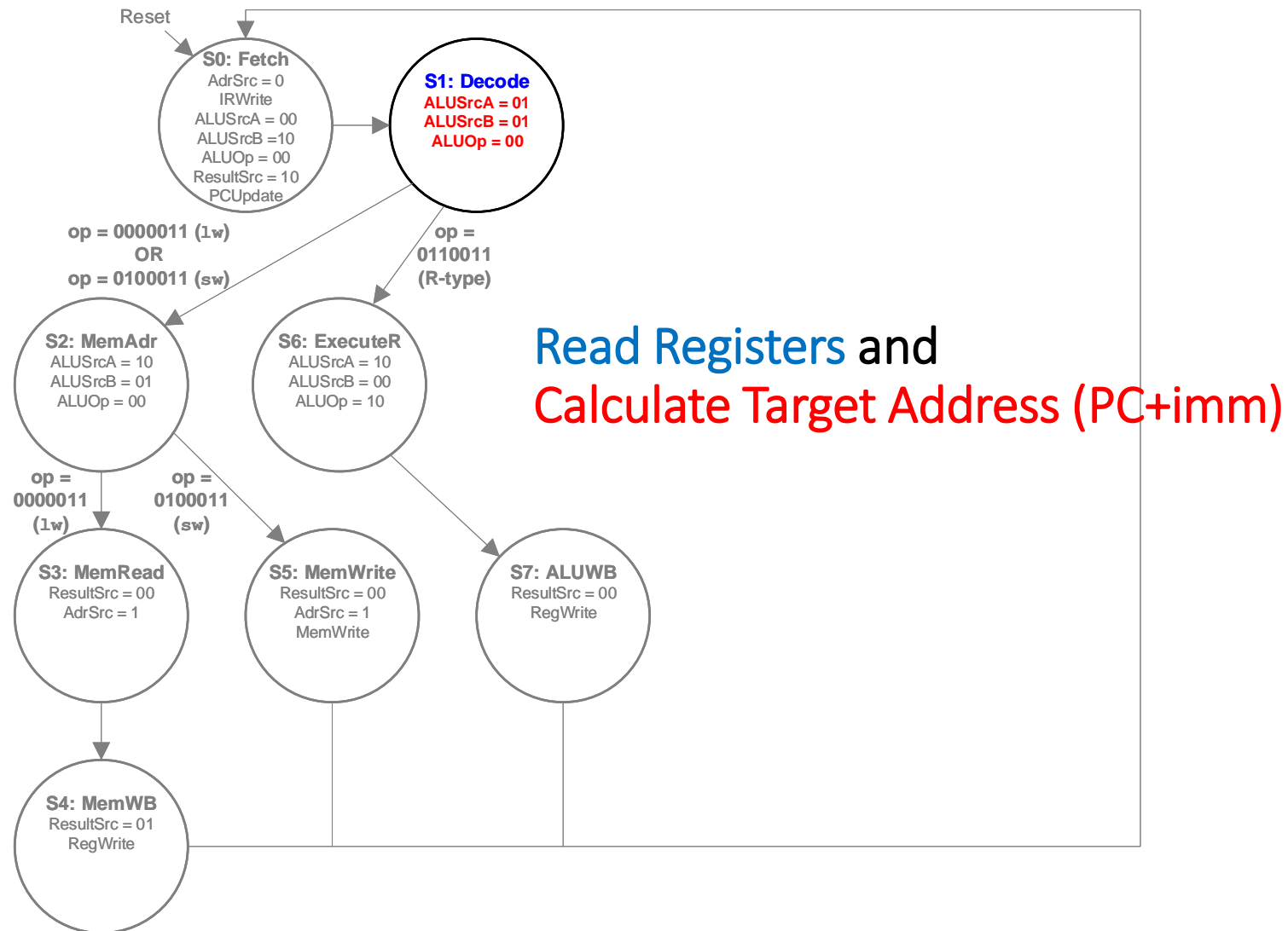


Main FSM: Decode (Target Address)

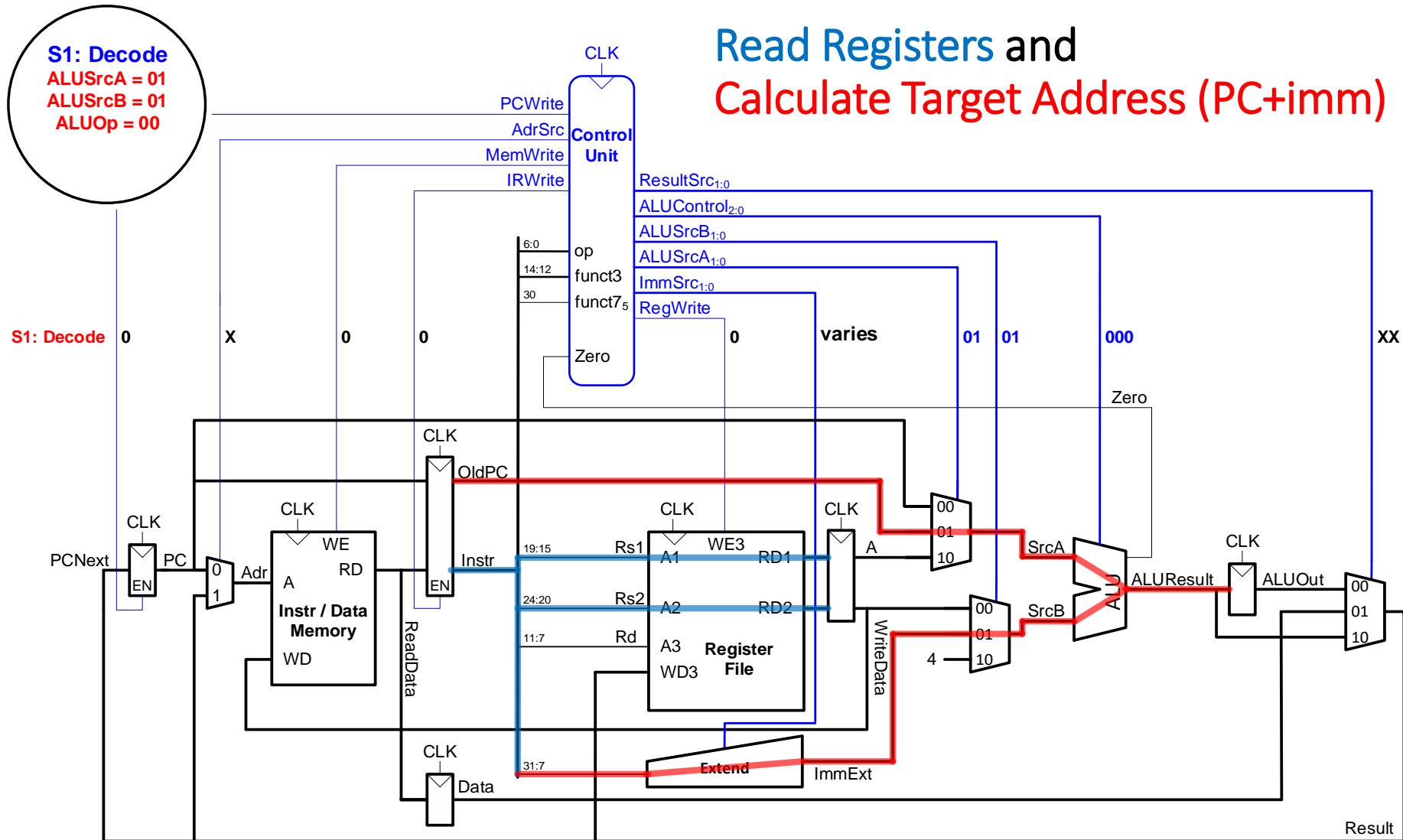

Main FSM: beq

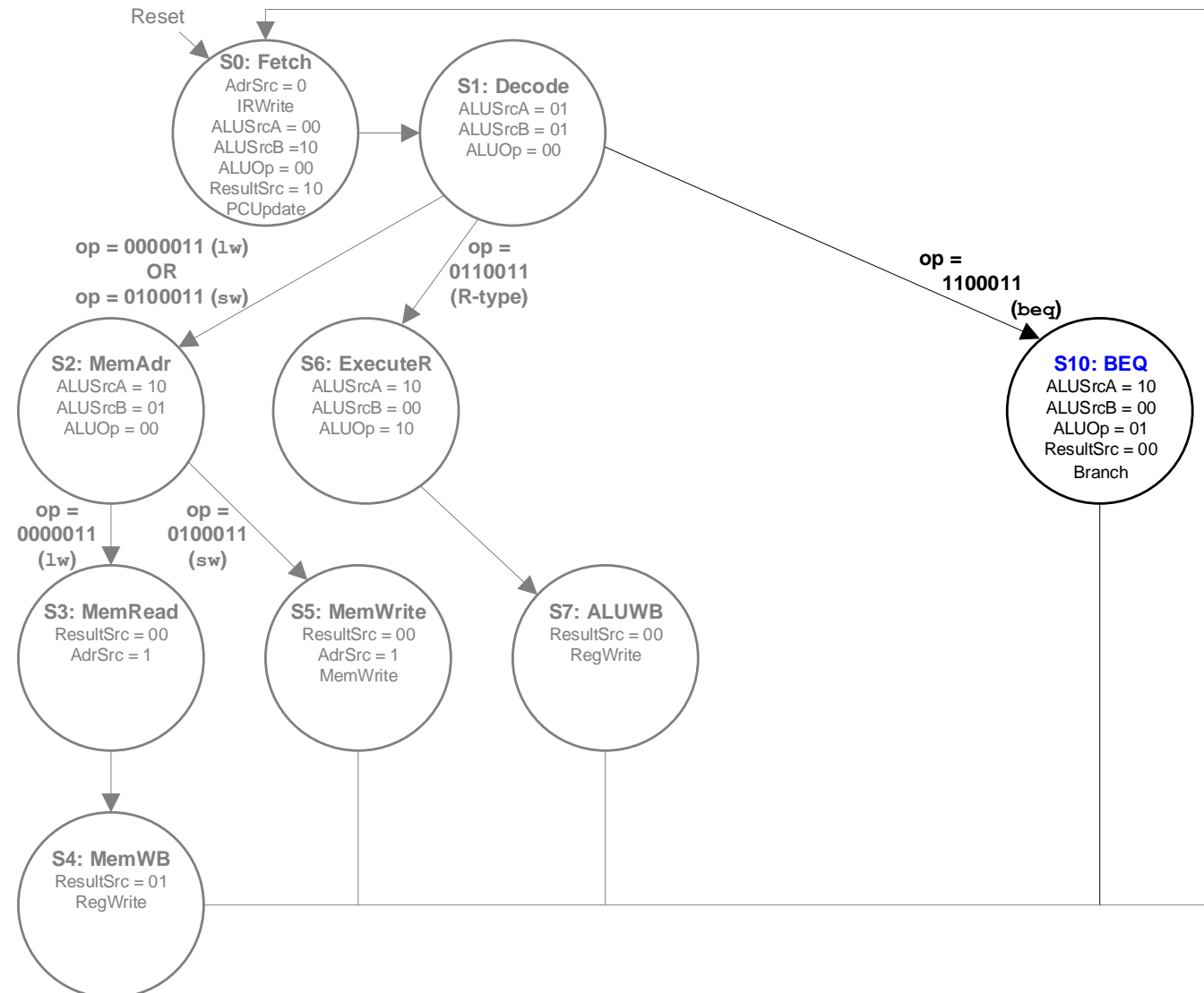


Main FSM: beq Datapath

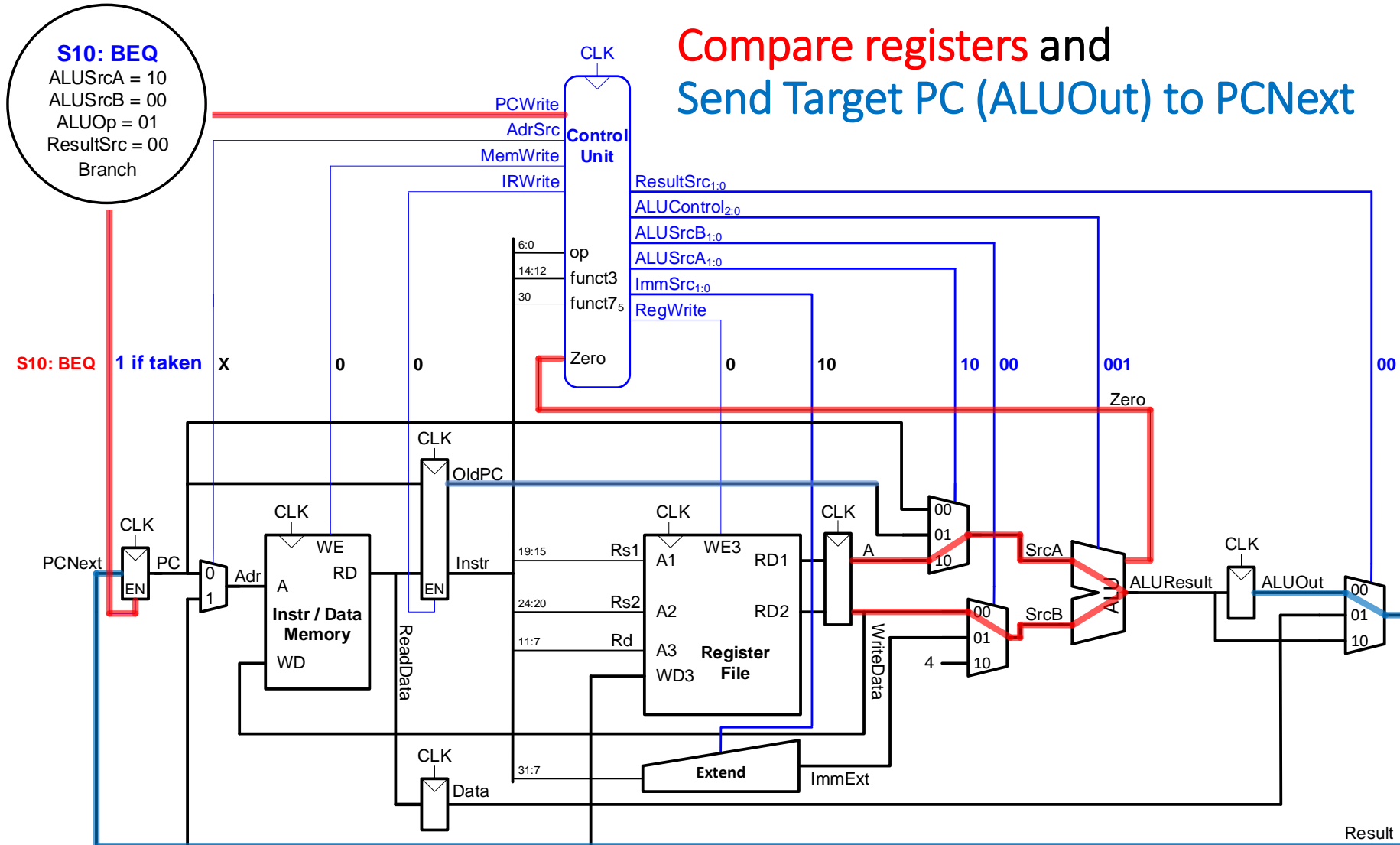


Chapter 7: Microarchitecture

Extending the RISC-V Multicycle Processor


Main FSM: I-Type ALU Execute

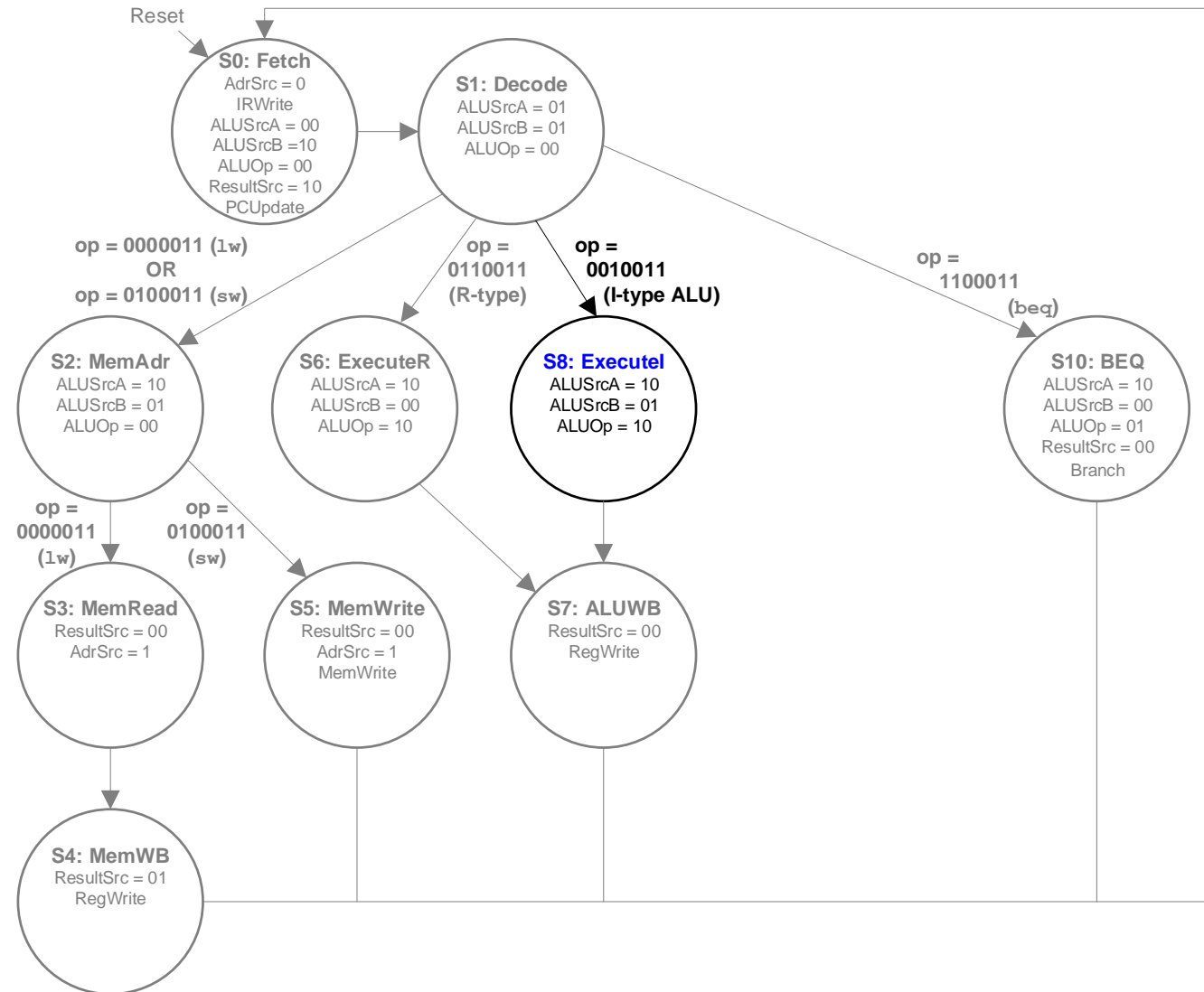


Main FSM: I-Type ALU Exec. Datapath

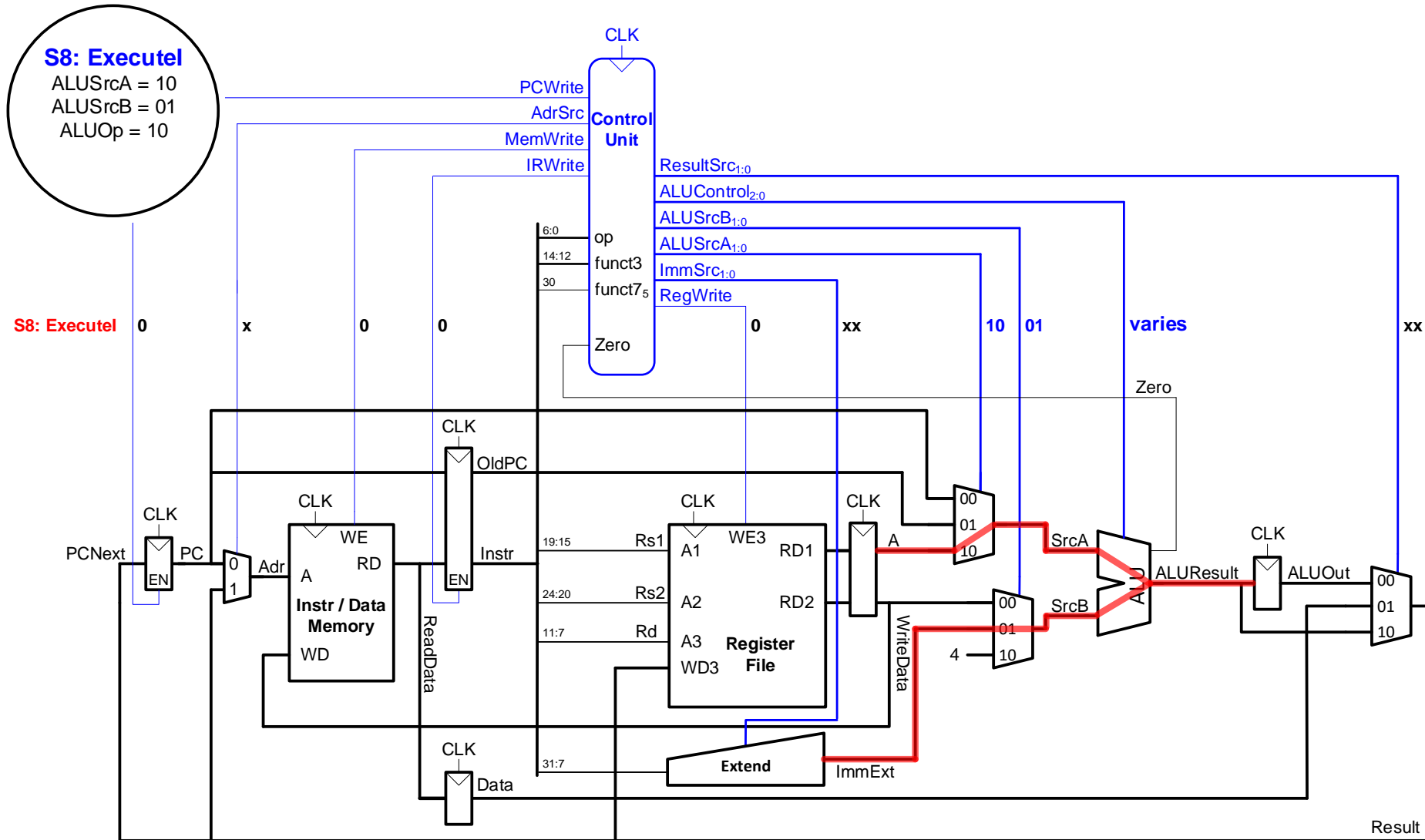

Main FSM: jal

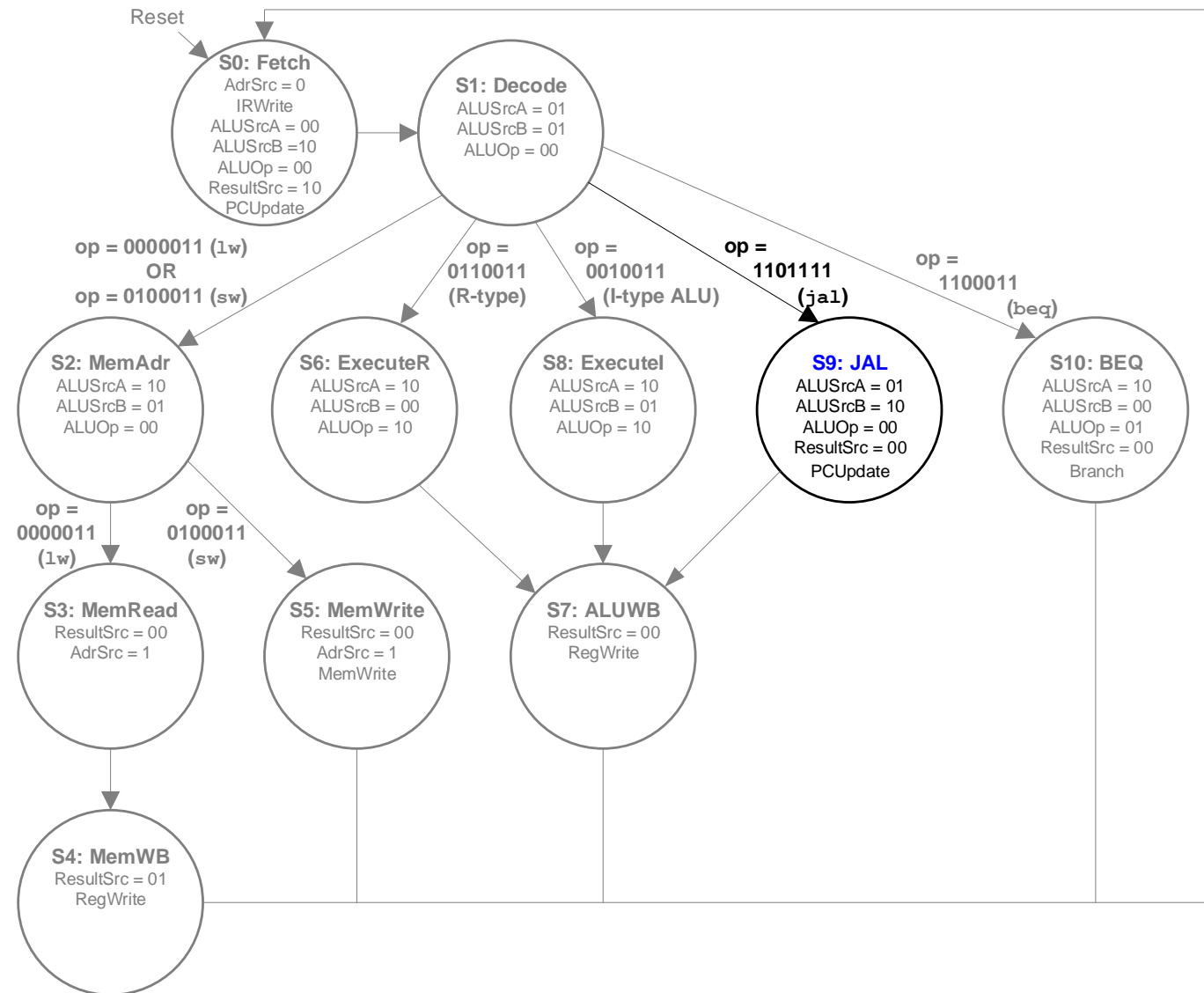


Main FSM: jal Datapath

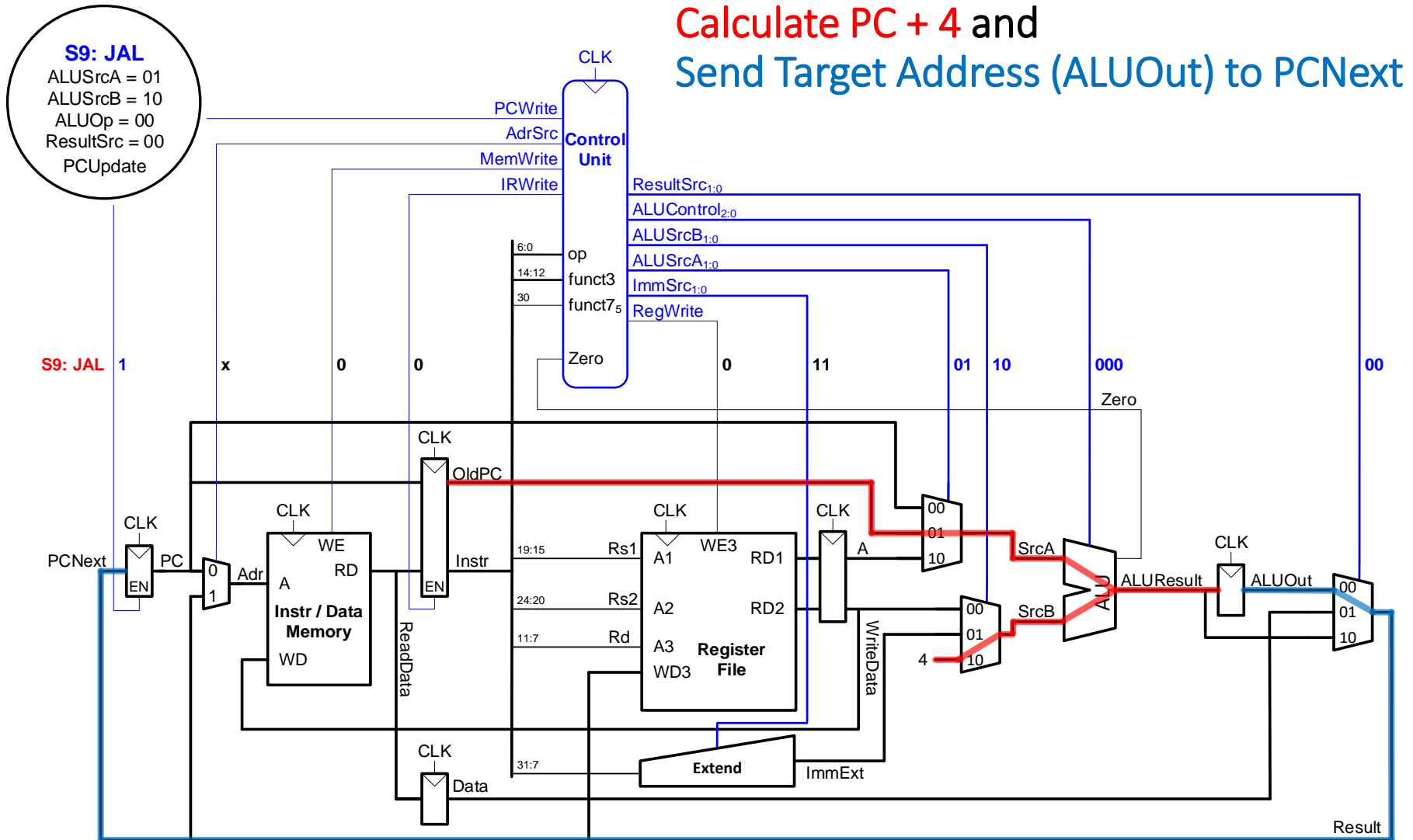

Main FSM: jal

PC + 4 is
written to rd
in **S7: ALUWB**

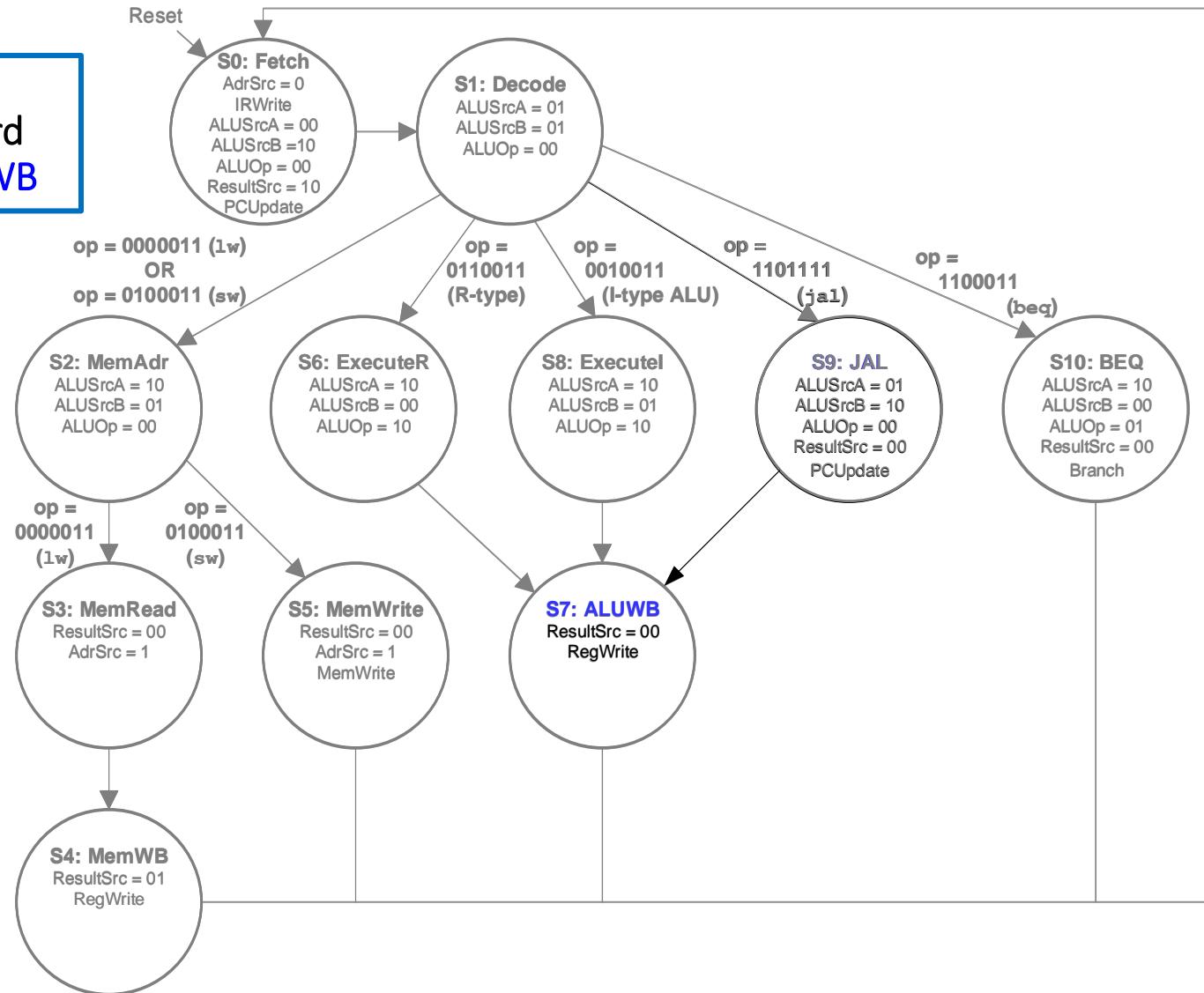

Multicycle Processor Main FSM

State	Datapath μ Op
Fetch	Instr \leftarrow Mem[PC]; PC \leftarrow PC+4
Decode	ALUOut \leftarrow PCTarget
MemAdr	ALUOut \leftarrow rs1 + imm
MemRead	Data \leftarrow Mem[ALUOut]
MemWB	rd \leftarrow Data
MemWrite	Mem[ALUOut] \leftarrow rd
ExecuteR	ALUOut \leftarrow rs1 op rs2
ExecuteI	ALUOut \leftarrow rs1 op imm
ALUWB	rd \leftarrow ALUOut
BEQ	ALUResult = rs1-rs2; if Zero, PC \leftarrow ALUOut
JAL	PC \leftarrow ALUOut; ALUOut \leftarrow PC+4

