

Switching Circuits and Switching Expressions

Two Types of Switches

Normally Open Switch

Normally Closed Switch

Two Types of Connections

Series Connection

Parallel Connection

EX-OR

Majority of 3

$F(x,y,z) =$ 1 when two or more inputs are 1's
 0 otherwise

Series-Parallel Switching Circuits

- Building Blocks
 - Normally open switch
 - Normally closed switch
- Composition Rules
 - Series
 - Parallel

Are these primitives sufficient to implement any Boolean function?

Synthesis of Series-Parallel Switching Circuits

- From Truth Tables

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Synthesis of Series-Parallel Switching Circuits

- From Expressions

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

- Canonical Sum-of-Products (SOP) Expressions

$$F = A'BC' + A'BC + AB'C' + AB'C + ABC$$

- Minimal SOP Expressions, usually obtained by the K-map Method

		B,C			
		00	01	11	10
A	0	0	0	1	1
	1	1	1	1	0

$$F = AB' + BC + A'B$$

- Nested Expressions

$$F = AB' + B(C + A')$$

Nested AND-OR Expressions

Any nested AND-OR expression of positive and negative variables can be implemented as a series-parallel switching network.

Given variables $x_1, x_2, \dots$

x_i is an expression

x_i' is an expression

If F and G are expressions, then

$(F.G)$ is an expression

$(F+G)$ is an expression

Examples

$$F = ((a'.b)+(c.(a'+d')))$$

$$F = a'b + c(a'+d')$$

$$G = (xyz + y'z + y)u$$

$$H = (a.b).(c.d)+c'd$$

Notes:

Parentheses can be omitted
when there is no confusion.

. has precedence over +

. may be omitted when there is no confusion

General Boolean Expressions

General nested Boolean AND-OR-NOT expressions can be implemented after using the De Morgan's Laws to move all negations from subexpressions to variables.

De Morgan's Laws

$$(F+G+\dots)' = F'.G' \dots$$

$$(F.G\dots)' = F' + G' + \dots$$

Example

Consider $F = AB' + B(C + A')$

Suppose we wish to implement F' as a series-parallel switching circuit.

$$\begin{aligned} F' &= (AB' + B(C + A'))' \\ &= (A' + B).(B' + C'.A) \\ &= A'B' + ABC' \end{aligned}$$

Subcircuit Connection

Switch as a 3-terminal Device

Primitives

- Building Blocks
 - Normally open switch
 - Normally closed switch
- Composition Rules
 - Series
 - Parallel
 - Subcircuit

Sequential Circuits – Need Memory

Example: Dating Machine

On any given day, Jack and Jill can go on a date provided

- 1) they both agree to go on a date and
- 2) they did not go on a date on the day before

Primitives

- Building Blocks
 - Normally open switch
 - Normally closed switch
- Composition Rules
 - Series
 - Parallel
 - Subcircuit
- Memory

Implementation of switching circuits in a physical medium

Any medium which supports the primitives:

- Electromagnetic
- Hydraulic
- Pneumatic
- Solid-state electronic
 - Bipolar
 - Field-effect
-

Physical Characteristics

- Space
- Speed
- Power
- Reliability
- Cost
-

CMOS: Complementary Metal-Oxide Silicon